

19/09/22
Monday




(2) BEE (L)

① Concept of linearity & linear elements:-



The elements of a ckt is said to be linear if it follows the principle of homogeneity and the principle of superposition.

Homogeneity:- $f(a_1x_1 + a_2x_2) = a_1y_1 + a_2y_2$


x = input
 y = effect/output

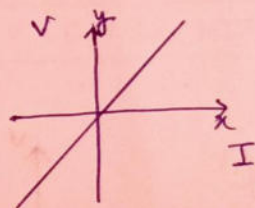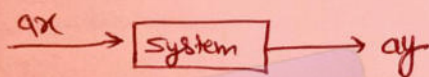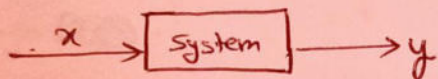

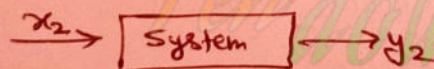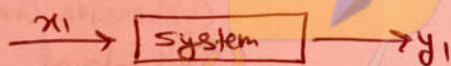Superposition:- $f(a_1x_1 + a_2x_2) = f(a_1x_1) + f(a_2x_2)$



(⊕ Addition)

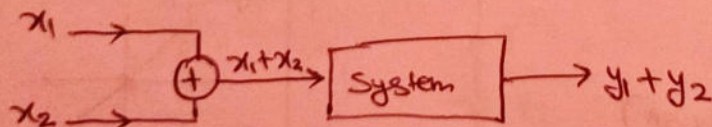



Eg. of linear elements:- Resistor, Inductor, Capacitor

② Unilateral and bilateral elements:-


A network is said to be bilateral if it allows the current to flow in both the directions by providing the same impedance.

Eg: Resistor is bilateral, capacitor, inductor, etc (to the current)

Eg of unilateral element → diode

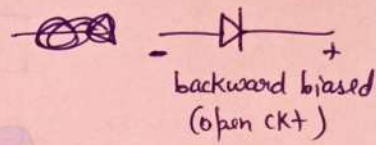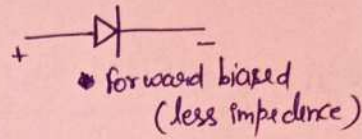

③ Eg ①

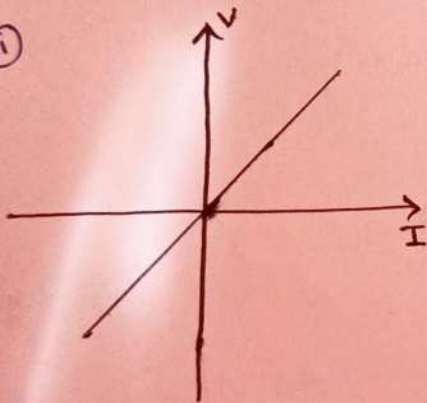


- ① Linear
- ② passive (ve characteristic of impedance)
- ③ bilateral

for active there will -ve characteristic of impedance

④ Eg ②

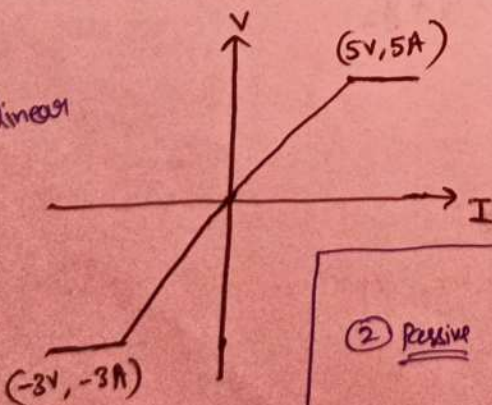~~Linear~~ Non-linear
~~passive~~
~~bilateral~~
unilateral



① Active elements → capable of delivering energy to ext. devices.

Eg) voltage & current sources

② Passive elements → capable of receiving energy or power.

Eg) R, C, L etc


④ Basic Circuit Law :- (2 laws)

- ① Kirchhoff's current law (KCL)
- ② Kirchhoff's voltage law (KVL)


① KCL :- At any junction / node the algebraic sum of the currents is equal to zero. i.e. Current entering the node = Current leaving the node

② KVL :- The algebraic sum of the voltage drops across various elements along with the algebraic sum of emf in any closed path is equal to zero.


$$\sum IR + \sum V = 0$$

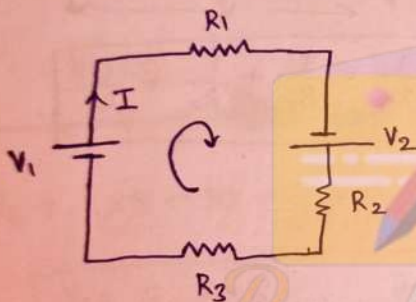

$$V_1 + V_2 = IR_1 + IR_2 + IR_3$$

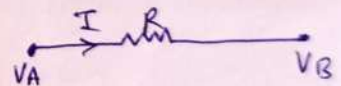

$$V_A - IR - V_B = 0$$

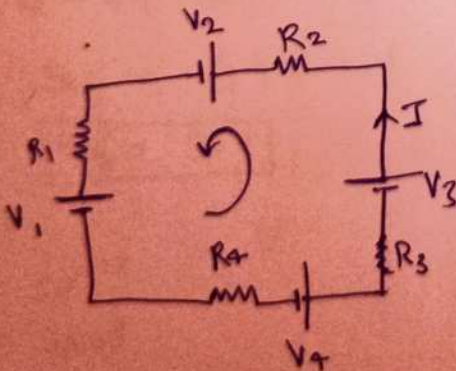


$$V_3 - IR_2 - V_2 - IR_1 - V_1 - IR_4 + V_4 - IR_3 = 0$$

$$V_3 + V_4 - V_1 - V_2 = I(R_2 + R_1 + R_3 + R_4)$$

⑤ current division & voltage drop

① Series ckt:-

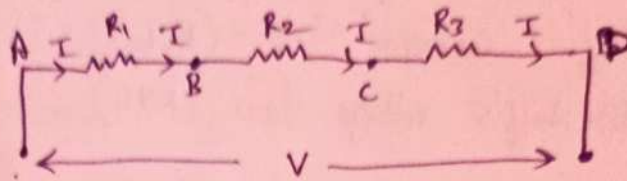
I = same in different elements,
but have diff. voltage drop.



$$R_{eq} = R_1 + R_2 + R_3$$

② Parallel ckt:-

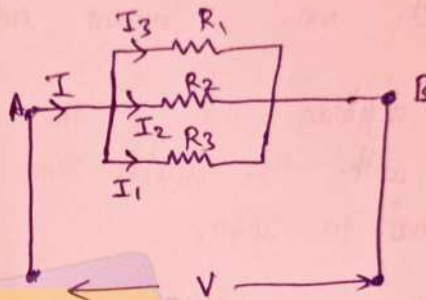current division and
voltage remains
constant.




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Pen down

20/09/22

③ BEE

Q1:-

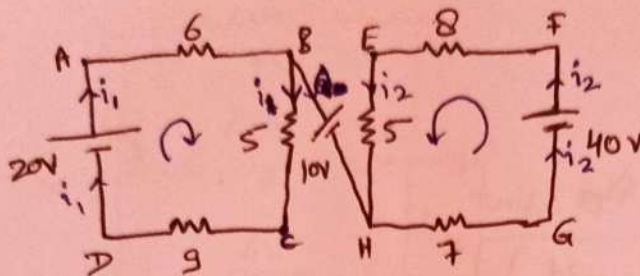

$$V_{CE} = ?$$

$$V_{AG} = ?$$

Solⁿ



$$20 = 20i_1$$

$$i_1 = 1A$$

$$40 = 20i_2$$

$$i_2 = 2A$$

Now by KVL

$$V_{CE} = V_C - V_E = i_1 \times 5 - 10 = 5V$$

$$V_C + i_1 \times 5 - 10 + i_2 \times 5 - V_E = 0$$

$$V_{CE} = -5V$$

that means E has higher pot than C

by KVL

$$V_A - 6i_1 - 10 - 7i_2 - V_G = 0$$

$$V_{AG} = 6 + 10 + 14$$

$$V_{AG} = 30V$$

② $i_2 = 5e^{-2t}$


$$i_4 = 3\sin t$$

$$v_3 = 4e^{-2t}$$

$$v_1 = ?$$

$$i_3 = 4 \times 2 \times (-2e^{-2t})$$

$$i_3 = -16e^{-2t}$$

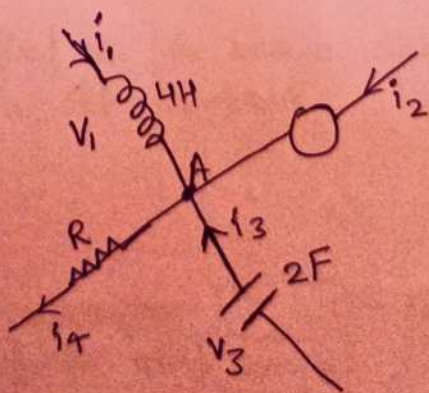

$$q = CV_3$$

$$i_3 = \frac{dq}{dt} = C \frac{dV_3}{dt}$$

using KCL

$$\sum I_A = 0$$

$$i_1 + i_2 + i_3 = i_4$$

$$5e^{-2t} + \cancel{i_1} - 16e^{-2t} = 3\sin t$$

$$i_1 = (3\sin t + 11e^{-2t})$$


$$\phi = Li$$

$$e = \frac{d\phi}{dt} = +L \frac{di}{dt}$$

$$e = 4 \left(3\cos t - 22e^{-2t} \right)$$

Pen down

Q1)

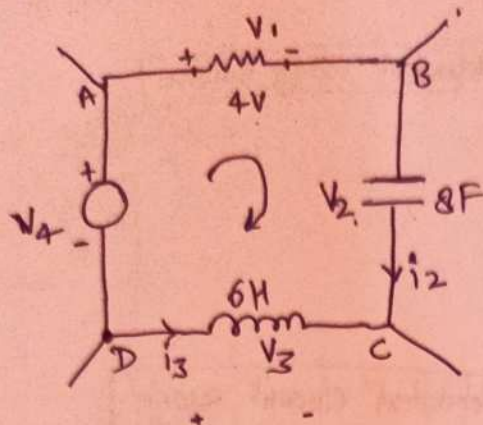

$$i_2 = ?$$

$$V_1 = 4V$$

$$i_3 = 2e^{-t/3}$$

$$V_4 = 4\cos 2t$$

sol) using KVL

[- to + is a rise
h to (true)]

$$V_4 - V_1 - V_2 + V_3 = 0$$

$$4\cos 2t - 4 - V_2 + 6 \frac{di_3}{dt} = 0$$


$$4\cos 2t - 4 + 6 \left(\frac{2}{3} e^{-t/3} \right) = V_2$$

$$i_2 = C \frac{dV_2}{dt} = 8 \left[\frac{d}{dt} (4\cos 2t - 4 + 4e^{-t/3}) \right]$$

$$i_2 = 8 \left[-8\sin 2t - \frac{4}{3} e^{-t/3} \right]$$


Dependent Sources: DS are defined as the source which depends upon the other parameters of a ckt or network.

(a) + o

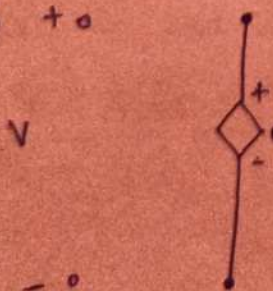


~~(dependent voltage source)~~
voltage dependent voltage source

(b)

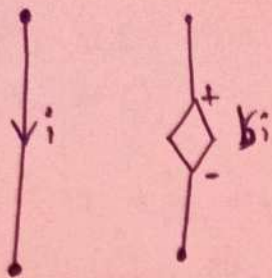


Current dependent voltage source

(c)

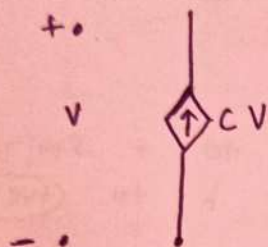


Voltage dependent current source

(d)

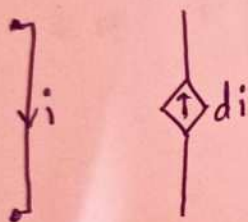


Current dependent current source

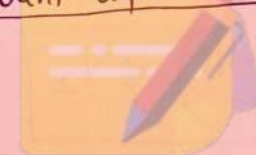


Pen down

dependent sources d.m.e

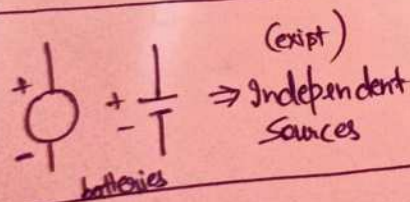

ques

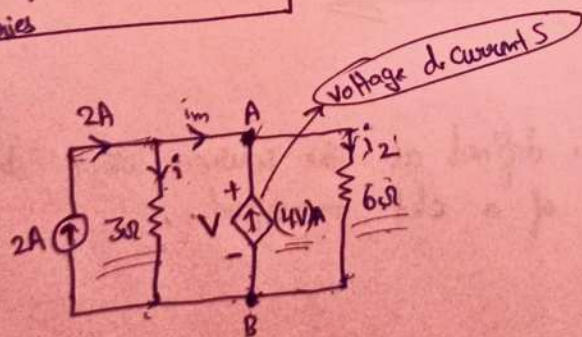

$V = ?$
 $i_1 = ?$
 $i_2 = ?$

Solⁿ


$$V_{AB} = 4V$$

$$i_2 = \frac{V_{AB}}{R_{AB}} = \frac{4}{6}$$

by KVL

$$3i = \frac{V}{6} \times 6$$

$$i = \frac{V}{3} \text{ A}$$

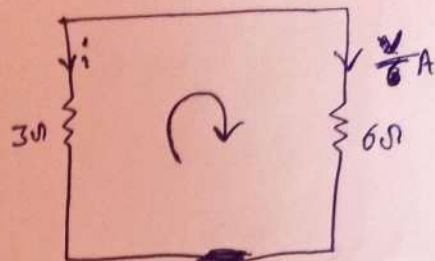

$$i_m = i_2 - 4V$$

$$2 = i + i_m = \frac{V}{3} + \frac{V}{6} - 4V$$

$$2 = \frac{V}{2} - 4V$$

$$4 = V - 8V$$

$$V = \frac{-4}{7}$$

$$4V = \frac{-16}{3}$$

$$i = 4V - i_2 + 2$$

$$\frac{V}{3} = 4V - \frac{V}{6} + 2$$

$$\frac{V}{6} = 6V + 2$$

Mesh Analysis:-

~~KCL in mesh 1~~

KCL

$$i + i_2 = i_1$$

KVL in mesh 1

$$V_1 - i_1 R_1 - i R_2 - i_1 R_3 = 0$$

$$V_1 = i_1 R_1 + i_1 R_3 + i R_2$$

$$V_1 = i_1 R_1 + i_1 R_3 + i_1 R_2 - i_2 R_2$$


$$V_1 = i_1 (R_1 + R_2 + R_3) - i_2 R_2$$

KVL in mesh 2

$$-V_2 - i_2 R_5 + i R_2 - i_2 R_4 = 0$$

$$V_2 = i R_2 - i_2 R_5 - i_2 R_4$$

$$V_2 = -i_2 (R_4 + R_5 + R_2) + i R_2$$

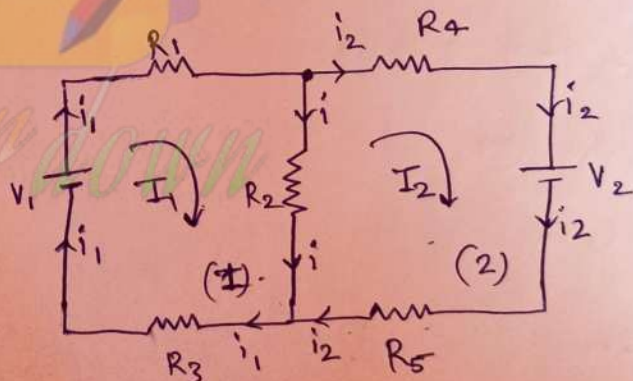

26/09/22

BEE

★ Mess analysis using Matrix form :- (Analog to KVL)

Mesh I:-

$$V_1 - I_1 R_1 - (I_1 - I_3) R_3 - (I_1 - I_2) R_2 = 0$$

$$I_1 (R_1 + R_2 + R_3) - I_2 R_2 - I_3 R_3 = V_1 \quad \text{--- (i)}$$

Mesh II:-

$$V_2 - (I_2 - I_1) R_2 - (I_2 - I_3) R_5 - I_2 R_4 = 0$$

$$-I_1 (R_2) + I_2 (R_2 + R_5 + R_4) - I_3 R_5 = V_2 \quad \text{--- (ii)}$$

Mesh III:-

$$V_3 - (I_3 - I_2) R_5 - (I_3 - I_1) R_3 - I_3 R_7 = 0$$

$$-I_1 R_3 - I_2 R_5 + I_3 (R_5 + R_3 + R_7) = V_3 \quad \text{--- (iii)}$$

\therefore in matrix form -

$$\begin{bmatrix} R_1 + R_2 + R_3 & -R_2 & -R_3 \\ -R_2 & R_2 + R_4 + R_5 & -R_5 \\ -R_3 & -R_5 & R_5 + R_3 + R_7 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix}$$

(i) Calculate Δ

$$(ii) \Delta_1 \begin{bmatrix} V_1 & R_{12} & R_{13} \\ V_2 & R_{22} & R_{23} \\ V_3 & R_{32} & R_{33} \end{bmatrix}$$


(iii) Δ_2

(iv) Δ_3


$$I_1 = \frac{\Delta_1}{\Delta}$$

$$I_2 = \frac{\Delta_2}{\Delta}$$

$$I_3 = \frac{\Delta_3}{\Delta}$$

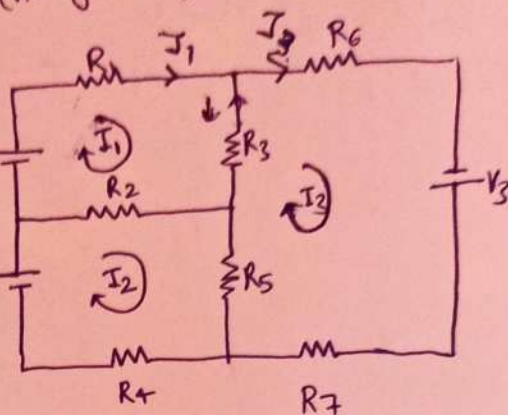

★ Nodal analysis 1- (similar to KCL)

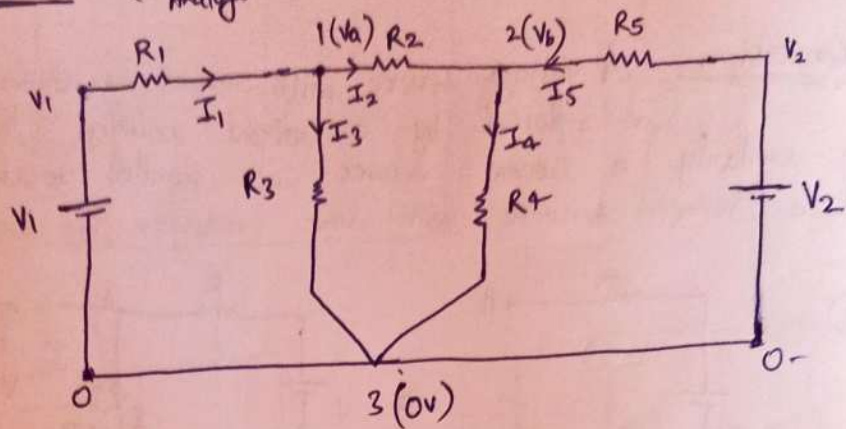

KCL at Node 1:

$$I_3 = I_1 - I_2$$

$$I_1 = I_2 + I_3$$

$$\frac{V_a - V_1}{R_1} = \frac{V_a - V_b}{R_2} + \frac{V_a - 0}{R_3}$$

At node 2:

$$I_4 = I_2 + I_5$$


$$\frac{V_b - 0}{R_4} = \frac{V_a - V_b}{R_2} + \frac{V_2 - V_b}{R_5}$$

Star:



Short ckt
Same polarity connected

Delta:



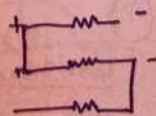


Diff'n polarity



Connected to 3 resistors,

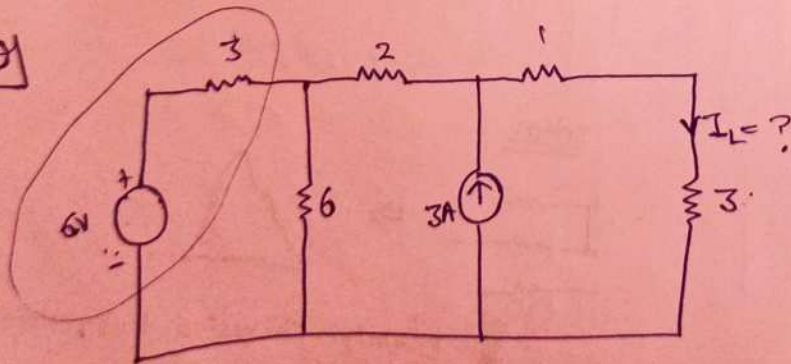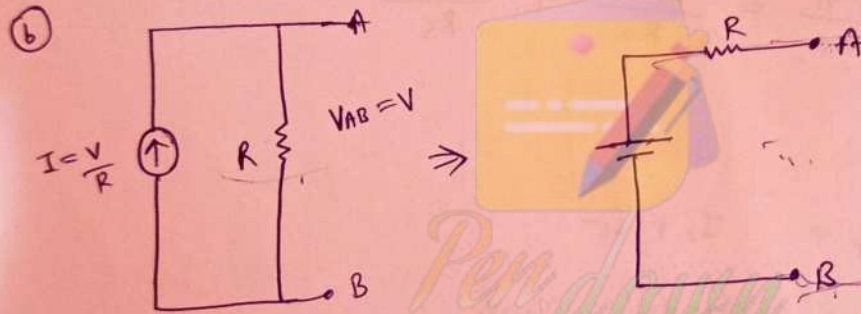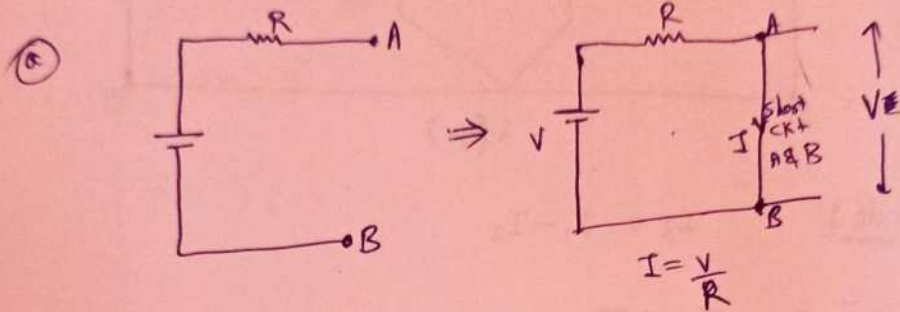① Source Conversion:- A voltage source with series resistance can be converted or replaced by a current source with same resistor in parallel. Similarly a current source with parallel resistor can be converted a voltage source with same resistor in series.






$$I_1 = \frac{6}{3} = \frac{2}{3} \text{ A}$$

$$11\Omega \oplus I = \frac{2}{3} \text{ A}$$

$$V = \frac{22}{3} \text{ V}$$

$$\frac{11}{3} \text{ A}$$



Converted
resistor in

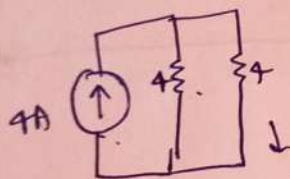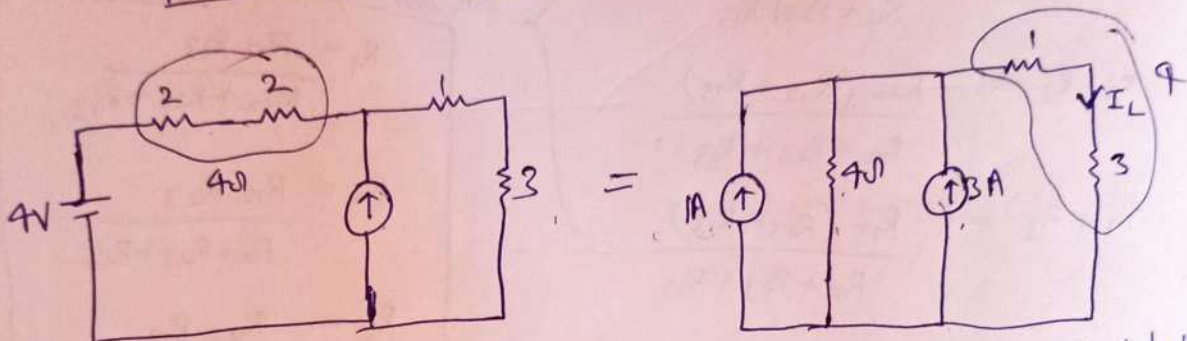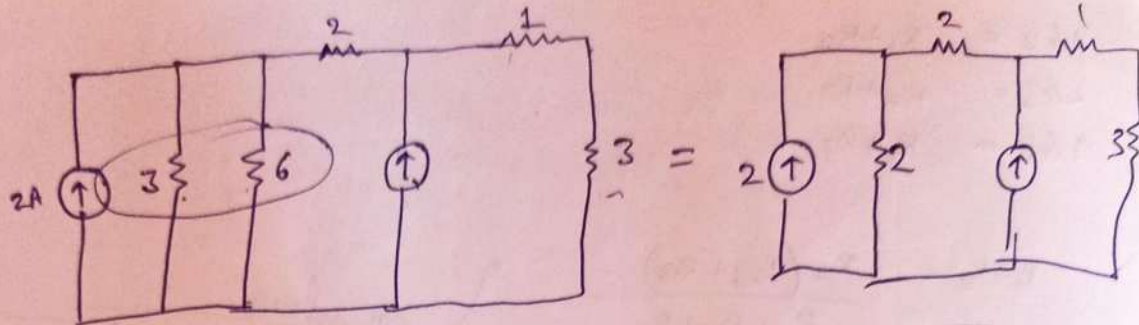

Current division rule

Since Resistance of both paths
are equal so
 $I_L = 2A$ i.e. $\left(\frac{3+1}{2}\right)A$

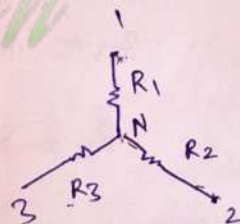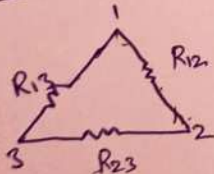② Delta to Star Conversion
($\Delta, D/d$)




Y form, y

$$182 = \frac{R_{12}(R_{23} + R_{13})}{R_{12} + R_{23} + R_{13}}$$

$$263 = \frac{R_{23}(R_{12} + R_{13})}{R_{12} + R_{23} + R_{13}}$$

$$361 = \frac{R_{13}(R_{23} + R_{12})}{R_{12} + R_{23} + R_{13}}$$

In delta
both are same

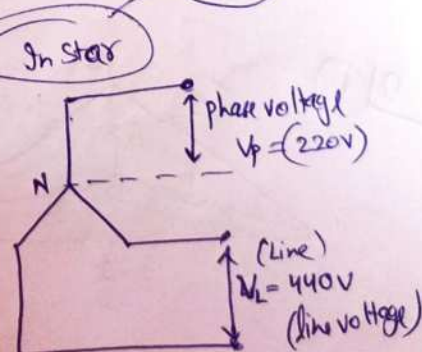

$$V_L = \sqrt{3}V_p$$

$$\frac{2}{3}A$$

$$\frac{11}{3}A$$

$$\frac{11}{3}A$$

$$1 \& 2 = R_1 + R_2$$

$$2 \& 3 = R_2 + R_3$$

$$1 \& 3 = R_1 + R_3$$

$$R_1 + R_2 = \frac{R_{12} (R_{23} + R_{13})}{R_{12} + R_{23} + R_{13}}$$

$$R_2 + R_3 = \frac{R_{23} (R_{12} + R_{13})}{R_{12} + R_{23} + R_{13}}$$

$$R_1 + R_3 = \frac{R_{13} (R_{12} + R_{23})}{R_{12} + R_{23} + R_{13}}$$

on solving

$$R_1 = \frac{R_{12} R_{13}}{R_{12} + R_{23} + R_{13}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{13}}$$


$$R_3 = \frac{R_{23} R_{13}}{R_{12} + R_{23} + R_{13}}$$

★ Star → Delta

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$
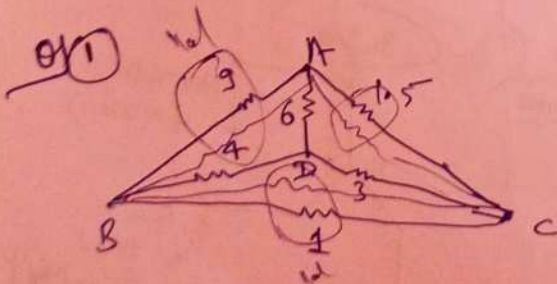
$$R_{13} = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$



$$R_{AB} = ?$$

$$R_{BC} = ?$$

$$R_{AC} = ?$$