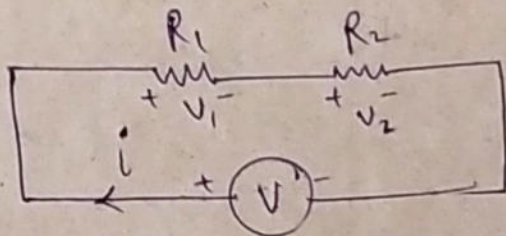


## Voltage division rule:

→ applied for series combin<sup>n</sup> as in series veld. divider.




$$i = \frac{V}{R_1 + R_2} \quad \therefore V_1 = iR_1 = \frac{VR_1}{R_1 + R_2}$$

$$V_2 = iR_2 = \frac{VR_2}{R_1 + R_2}$$

i.e.,  $V_{\text{resistor}} = \left[ \frac{\text{total voltage} \times \text{that resistor}}{\text{Equivalent resistance in series or sum of resist}} \right]$
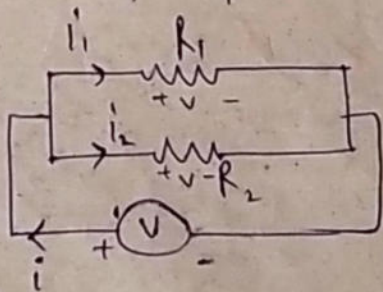
## Current division rule:

→ applied for parallel combin<sup>n</sup> as in parallel, current divider.



$$i = i_1 + i_2$$

$$i = \frac{V}{R_{eq}} \neq \frac{V(R_1 + R_2)}{R_1 R_2}$$

$$i_1 = \frac{V}{R_1}, \quad i_2 = \frac{V}{R_2}$$

$$\begin{aligned} V &= iR_1 \\ V &= i_1 R_1 \\ iR_1 &= i_1 R_1 \end{aligned}$$

$$i_1 = \frac{1}{R_1} [iR_{eq}] \Rightarrow \frac{1}{R_1} \left[ \frac{V(R_1 + R_2)}{R_1 R_2} \times (i_1 + i_2) \right]$$



$$i_1 = \frac{i}{R_1} \frac{R_1 R_2}{R_1 + R_2} \Rightarrow i_1 = \frac{iR_2}{R_1 + R_2}$$

$$i_2 = \frac{1}{R_2} (i R_{eq}) = \frac{1}{R_2} \left( i \times \frac{R_1 R_2}{R_1 + R_2} \right)$$

$$i_2 = \frac{i R_1}{(R_1 + R_2)}$$

i.e.  $i_{resistor} = \left[ \frac{\text{total current} \times \text{opposit. resistance}}{\text{Sum of resistances}} \right]$

Q<sub>2</sub> Find Req.  
b/w a & b.

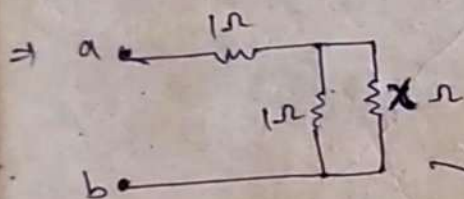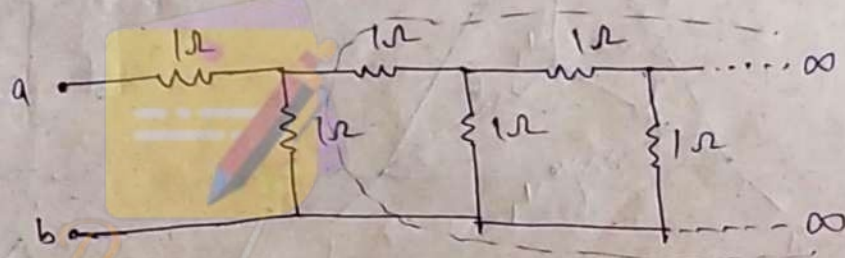

$$R_{eq} = \frac{1 \times x}{1+x} + 1$$

$$R_{eq} = x \Omega$$

$$x = \frac{x}{1+x} + 1$$

$$\Rightarrow x - 1 = \frac{x}{1+x} \Rightarrow x^2 - 1 - x = 0$$

$$x^2 - x - 1 = 0$$

$$\Rightarrow x = \frac{1 \pm \sqrt{1+4}}{2} \Rightarrow x = \frac{1 \pm \sqrt{5}}{2}$$

$$x = \frac{1 + \sqrt{5}}{2} \Omega$$



# Equivalent resistance using symmetry


## Vertical symmetry (mirror)

Points on V. plane have same potential  
Branches which are mirror ing. about V.P. have same current.


## Horizontal symmetry (folding)

all points which are mirror ing. about HORIZ. plane have same pot.


Q. 1

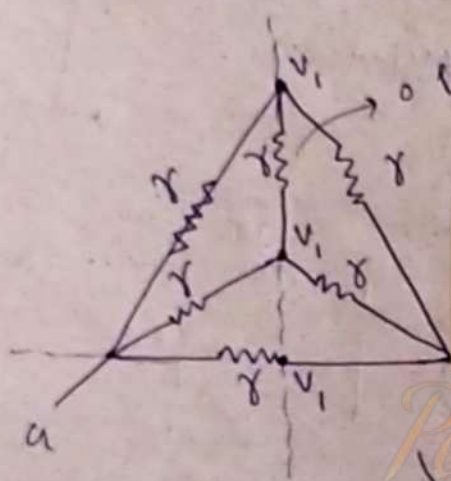

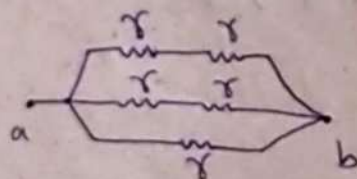clearly H.P. about a-b doesn't possess symmetry but V.P. does.




$$R_{eq} = \frac{\gamma}{2}$$

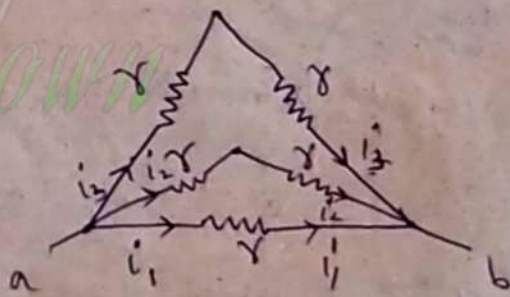

it passes both H.P.s & V.P.s.

Q. 2

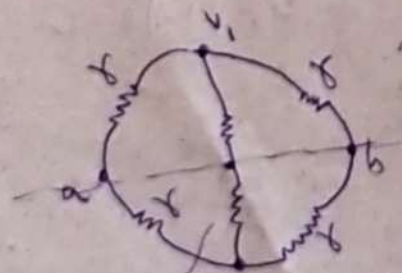


P.D. = 0  
∴ no current through this branch



$$R_{eq} = \gamma$$


So, basically, for this symmetry to hold, on that plane is same x & x

Q. 2

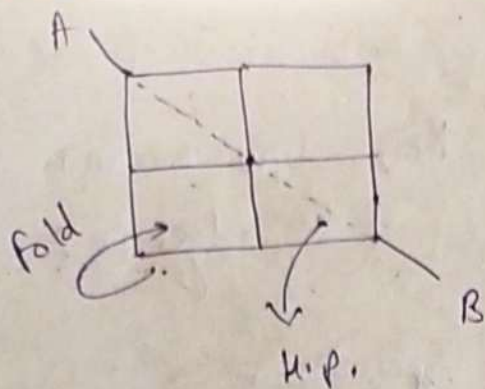


each small side have Resist. =  $R$   
 then Req across A-B?

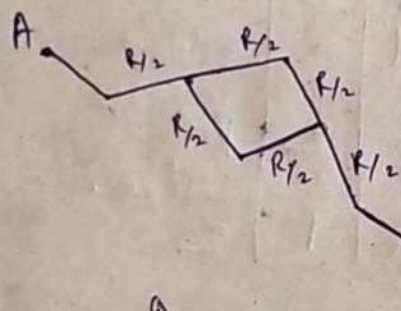→ let us use H.P.'s as Folding symmetry i.e.,  
 fold about H.P. & ~~not~~ each  $R \rightarrow \frac{R}{2}$



$\Rightarrow R_{eq} = \frac{3R}{2} //$

Q. 2

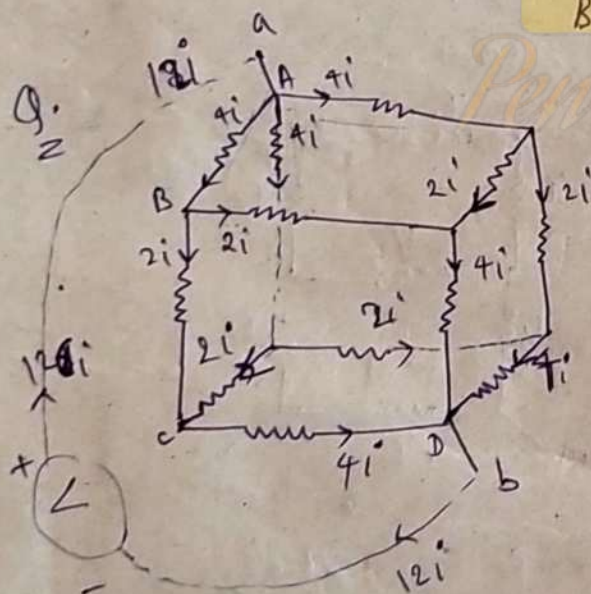

each resist. value =  $x$   
 find Req (a-b)?

apply KVL along the ~~open~~ closed path aABCDba

$V_a - 4i - 2i - 4i = V_b$

$V - 4ix - 2ix - 4ix = 0$

$V = 10ix$

$V = 12ix_{eq}$


$12ix_{eq} = 10ix$

$x_{eq} = \frac{10}{12}x$   
 $\frac{5}{6}x$

$\Rightarrow \boxed{x_{eq} = \frac{5}{6}x}$



Q. 2

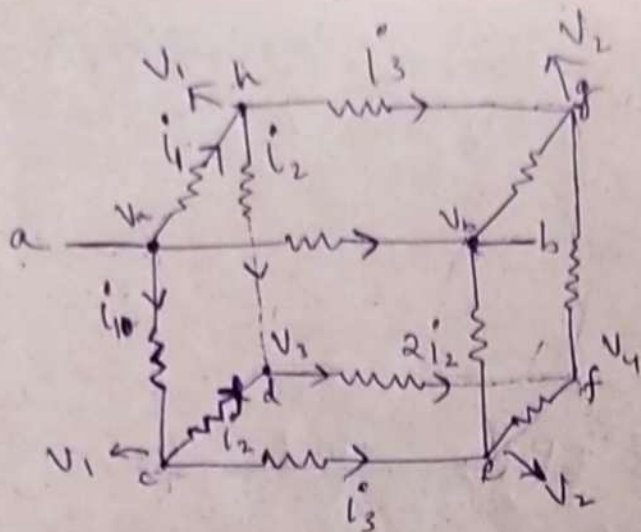



each resist. is  $= \gamma \Omega$

Req. b/w 2 corners of an edge is ?

$c \leftrightarrow h$  symm.  $\rightarrow$  equiv. pot.  $\rightarrow$   
 $e \leftrightarrow g$  symm.  $\rightarrow$  equiv. pot.  $\rightarrow$

	a	b
c	1	2
e	2	1
f	3	2
d	2	3
g	2	1
h	1	2

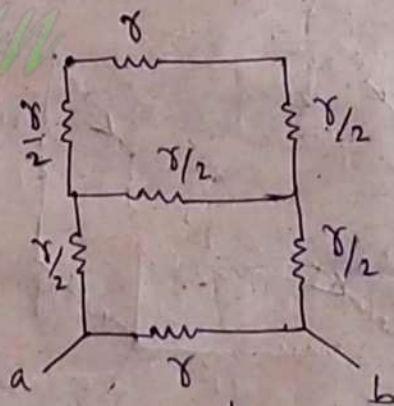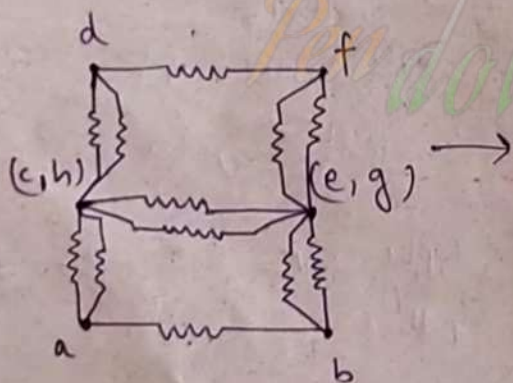$\rightarrow$  to avoid confusion  
 let's redraw the circuit.




$$\therefore R_{eq} = \frac{\frac{7\gamma}{8} \times \gamma}{\frac{7\gamma}{8} + \gamma \times \frac{5}{5}}$$


$$= \frac{7\gamma}{12}$$

$$\begin{aligned} & \frac{2\gamma \times \gamma}{2\gamma + \frac{\gamma}{2}} \\ & \frac{\frac{2\gamma \times \gamma}{5\gamma}}{\frac{2\gamma}{5} + \gamma} = \frac{2\gamma}{5} \\ & \frac{2\gamma}{5} + \gamma = \frac{7\gamma}{5} \end{aligned}$$

\* Star (Y) - delta (Δ) conversion

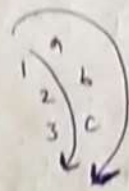

always

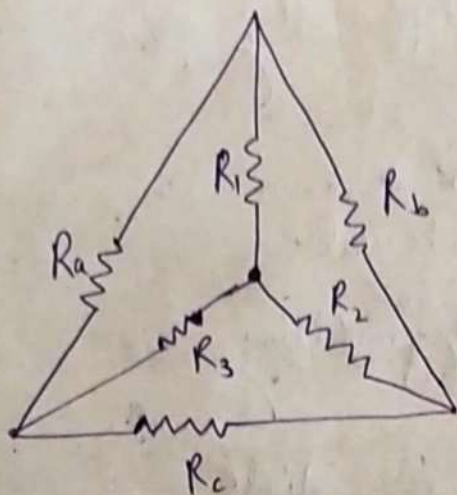

Δ to Y :

$$R_1 = \frac{R_a \cdot R_b}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_b \cdot R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a \cdot R_c}{R_a + R_b + R_c}$$

Y to Δ :

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$



## Active & Passive elements :

capable of delivering energy independently for an  $\infty$  duration of time.

or capable to supply an avg. power  $\neq 0$  to some ext. device, over an infinite time interval.

Hence, active elements are capable of providing power gain i.e.  $\left( \frac{\text{output power}}{\text{input power}} \neq 0 \right)$

ex.  $\geq$  volt. src, current src, transistor, op-Amp, diode etc.

Those which are not active are passive.

on short: Active  $\rightarrow$  energy donors.

Passive  $\rightarrow$  energy consumer.

$\rightarrow$  ex. inductor, resistor, capacitor, transformer etc.



## Bidirectional & unidirectional elements :

$\rightarrow$  Properties / characteristics are independent of the direction of current flow.

i.e.  $L \rightarrow R$  flow ho ya  $R \rightarrow L$  behaviour of element  $\rightarrow$  same.

ex.  $\geq$

Resistor

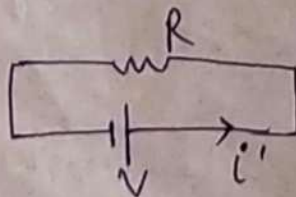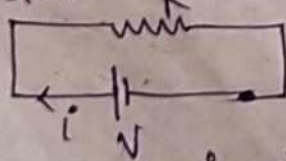


$$i = i' = \frac{V}{R}$$


means, in both cases resistance offered by resistor is same (independent of direction).

unidirectional → properties are direct dependant.

ex. diode

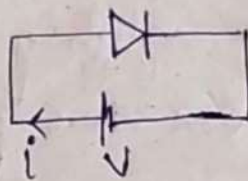





here  $i > 0$  i.e.  $R \rightarrow 0$

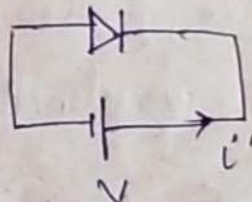

$i' \approx 0$  i.e.  $R \rightarrow \infty$

∴ Resistance (property) offered by diode in F.B direct<sup>n</sup> is nearly zero but in R.B, resist. offer is  $\rightarrow \infty$ .

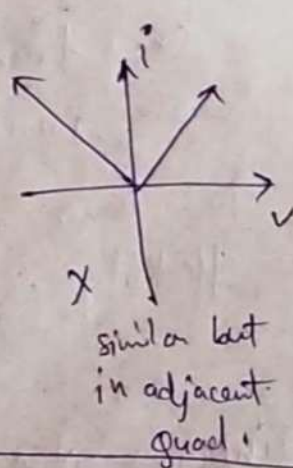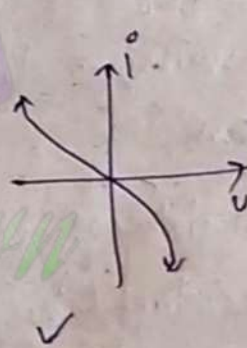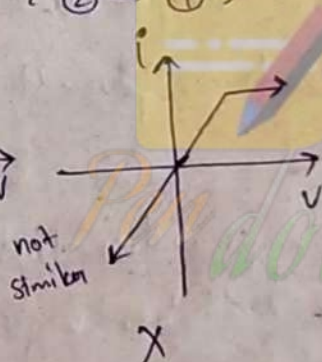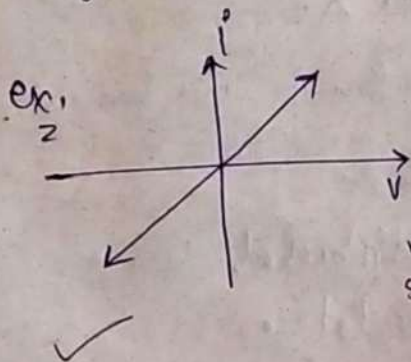Note: Bidirectional → characteristic curve is similar in opp. quadrants i.e.  $\{ \textcircled{1} \leftrightarrow \textcircled{3} \}$   
 $\{ \textcircled{2} \leftrightarrow \textcircled{4} \}$



Note:



$i < 0, v > 0$ $P < 0$ source → Active	$i > 0, v > 0$ $P > 0$ sink → consumer → Passive
$i < 0, v < 0$ $P > 0$ sink → Passive	$i > 0, v < 0$ $P < 0$ source → Active

source → energy lobe → -ve  
 sink → " accept → +ve

in short: whenever  $\frac{v}{i} < 0$

i.e. if slope  $< 0 \rightarrow$  Active

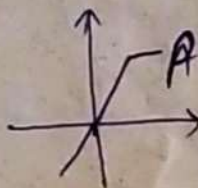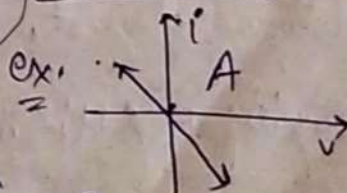Fails when resistance  $< 0$  in  
 ①<sup>st</sup> & ③<sup>rd</sup> Quadrant



ek bhi part  
 curve ka 'A' hai to  
 small 'A' laga lenge  
 $A \rightarrow -ve \text{ } \& \text{ } -ve \times -ve \rightarrow +ve$

due to this region its overall Active.




## lumped and distributed elements

↳ physical size of element is negligibly small when compared to wavelength of EM wave propagation.

ex. resistor, capacitor, inductor etc.
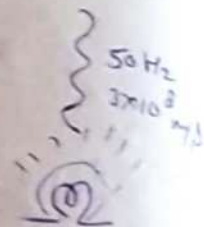
$$\lambda = \frac{v}{f} = \frac{3 \times 10^8}{50} = 6000 \text{ km}$$



50 Hz

∴ we assume all characteristic properties are concentrated in that small portion.

distributed → physical size is comparable to  $\lambda$ .

ex. transmission line from power station to our home  
or ~ 1000 km

to some resistance, inductance properties distributed have effect on entire line & can't be neglected.

## Linear & Non-linear elements:

↳ a linear relationship b/w excitation (i/p) & response (o/p).

ex. for a resistor,  $V \propto i \Rightarrow V = iR$

∴ resistor is linear element

• linearity = Homogeneity + Additivity

ex.  $\downarrow$   
 $\alpha V \rightarrow \alpha i$


$\downarrow$   
 $V_1 \rightarrow i_1$   
 $V_2 \rightarrow i_2$

then  $V_1 + V_2 \rightarrow i_1 + i_2$

for linearity both Homogeneity & additivity must be satisfied.

ohm's law → only for linear element ✓

ex. =

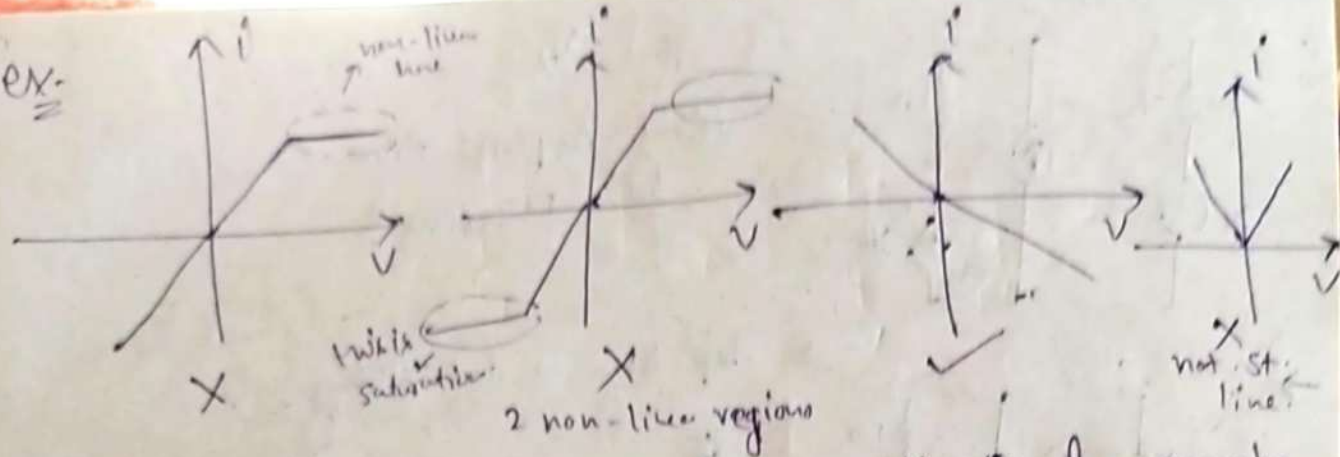

Note: every linear element must exhibit bidirectional property  
 $\therefore$  Graph must pass through origin + st. line + no saturation


### Circuit analysis theorems:

- Superposition
- Thevenin
- Norton
- Max. Power

All these are valid for bilateral, linear and lumped elements in circuit

① Superposition: volt./current across an element is alg. sum of volt./current in that element due to independent source acting alone at a time.

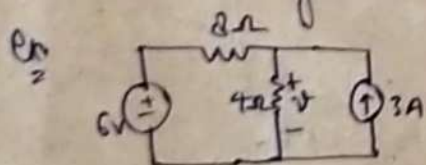
- apply when multiple sources are present.
- when considering 1<sup>st</sup> dep. src., replace all other dep. src by their Rint.



Find 'V' using superposition

Taking (6V) in consideration

Taking (3A) in consid<sup>n</sup>:

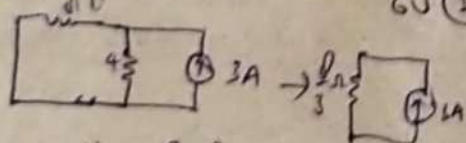

$$V_2 = 3 \times \frac{4 \times 8}{4 + 8} = 8V$$




$$i_1 = \frac{6}{12} = 0.5A$$

$$\therefore V_1 = 0.5 \times 4 = 2V$$

$$\therefore V = V_1 + V_2 = 10V$$




Q.2

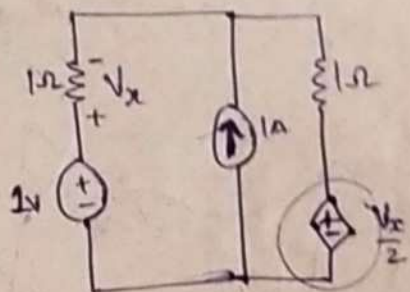


find  $V_x = ?$   
using superposition theorem?

dep. src  $\rightarrow$  do nothing.

$\rightarrow$

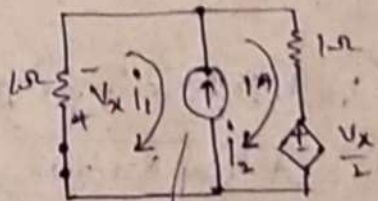

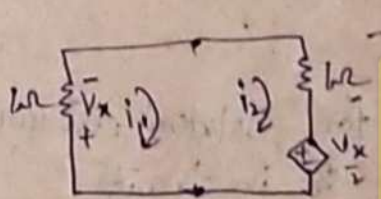current src b/w 2 meshes  $\rightarrow$  supermesh.



$$-i_1 - i_2 - \frac{V_x}{2} = 0$$

$$i_2 - i_1 = 1$$

$$V_x = i_1$$


$$-i_1 - i_2 - \frac{i_1}{2} = 0$$

$$-\frac{3i_1}{2} - (1 + i_1) = 0 \Rightarrow -\frac{3i_1}{2} - \frac{2}{2} - \frac{2i_1}{2} = 0$$

$$-5i_1 = 2 \Rightarrow i_1 = -\frac{2}{5}$$

$$V_x = -0.4V$$

then

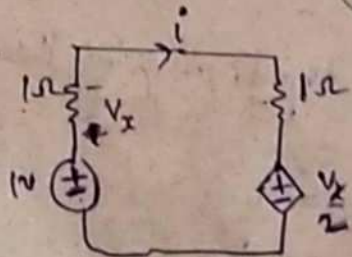

$$1 - V_x - i - \frac{V_x}{2} = 0$$

$$i = V_x$$

$$1 - 5V_x = 0 \Rightarrow V_x = 0.2V$$

$$V_x = V_{x1} + V_{x2} = 0V$$