

Power = rate of doing work i.e. rate of transfer of energy.

$$P = \frac{dw}{dt} \quad \text{J/s or Watt (W)} \quad [\text{Instantaneous power}]$$

$$W = \int_{t_1}^{t_2} P dt \quad \text{then} \quad P_{av.} = \frac{\text{total workdone}}{\text{total time}}$$

$$\text{i.e. } P_{av.} = \frac{1}{(t_2 - t_1)} \int_{t_1}^{t_2} P dt$$

Energy = Ability of doing work.

workdone per unit time is power and workdone for a 'time-interval' is equivalent to energy.

$$\text{i.e. } E = \int_{t_1}^{t_2} P dt = P \times t \quad \text{Joule (J)}$$

Potential difference = work done when a unit+ charge is moved from point 'a' to 'b' in presence of field of 'b'.



Electric potential difference doesn't depend on path chosen.

$$V_{ab} = V_a - V_b \rightarrow \begin{matrix} \text{a} & \text{b} \\ \downarrow & \downarrow \\ \text{Point 'a' at higher potential} & \text{'b' at lower potential} \end{matrix}$$

Potential difference or voltage across a & b

of course,  $V_{ab} = -V_{ba}$

Voltage gain and drop

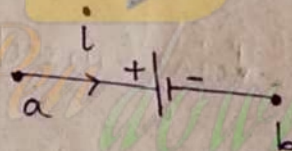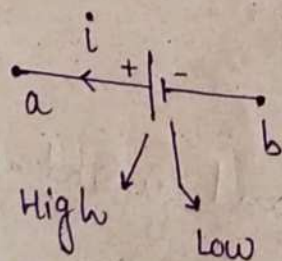


Remember!


① Low potential  $\rightarrow$  High potential  
voltage Gain

② High potential  $\rightarrow$  Low potential  
voltage drop

Representation  $\rightarrow$

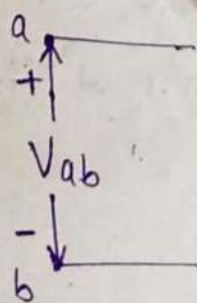

or

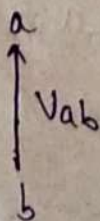

where

$$V_a > V_b$$



current - rate of flow of charge through a closed conducting path.

$$i_{av.} = \frac{\Delta q}{\Delta t} \quad \text{Ampere (A)}$$


$$i = \frac{dq}{dt} \quad \text{and} \quad q = \int_{t_1}^{t_2} i dt \quad (\text{charge transferred b/w } t_1 \text{ \& } t_2)$$

DC - unidirectional.


AC - cyclic  $\oplus$  half  $\rightarrow$   $\ominus$  half  $\rightarrow$   $\oplus$  half  $\rightarrow$   $\ominus$  half...

in both AC, DC magnitude may or may not be constant.

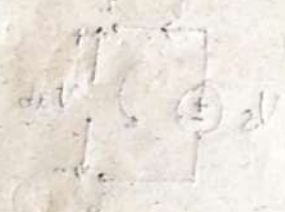
\* unless stated otherwise we consider constant magnitude



# Sources

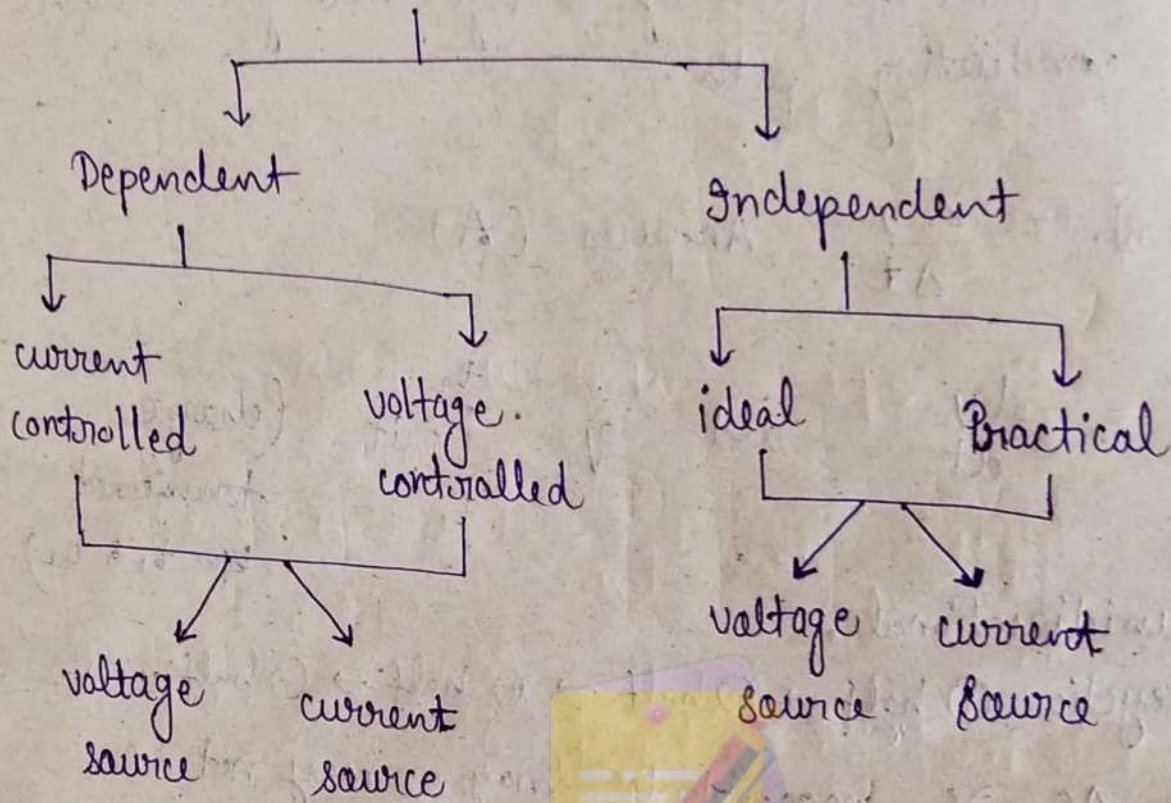

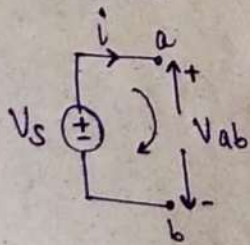
## \* Ideal and Practical voltage source -



using KVL,


$$V_s - V_{ab} = 0$$

$$V_s = V_{ab}$$

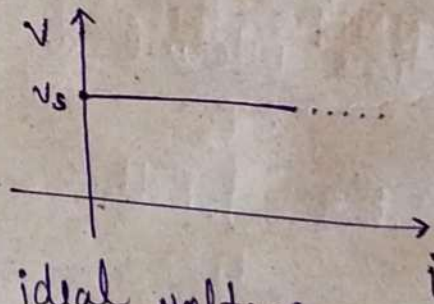

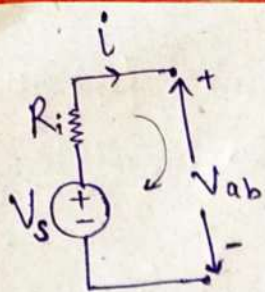• No internal resistance  $\therefore$  ideal voltage source delivers energy at a specified voltage which doesn't depend on current delivered by the source






using KVL;

$$V_s - iR_{int} - V_{ab} = 0$$

$$V_{ab} = -R_{int} i + V_s$$

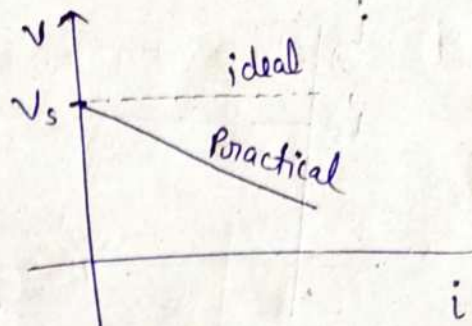

$\therefore$  in practical source,  $R_{int} \neq 0$  (finite)

so, it delivers the energy at a specified ~~rate~~ voltage which depends on current delivered by the source.

in short : Ideal  $\rightarrow$  Terminal voltage = source voltage  
 Practical  $\rightarrow$  Terminal voltage < source voltage

•  $V_{ab} \rightarrow$  terminal voltage



\* ideal and Practical current source -




$\downarrow$   
 •  $R_{int} \rightarrow \infty$

• delivers the energy at a specified current which doesn't depend on voltage source across.


$\downarrow$   
 •  $R_{int} \rightarrow \text{finite}$

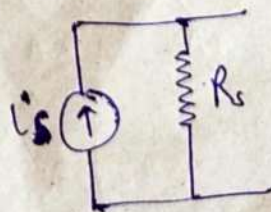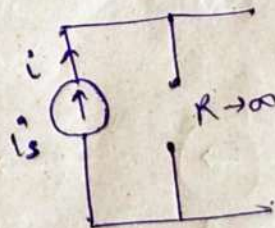• delivers the energy at a specified current which is dependent on voltage across the source



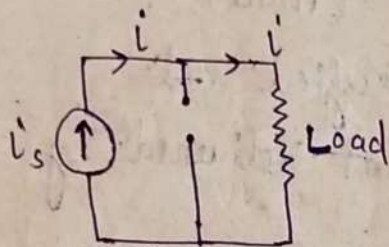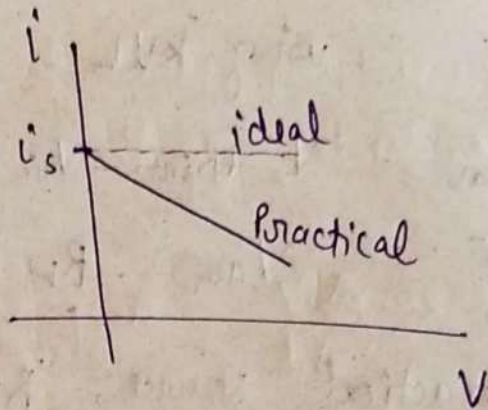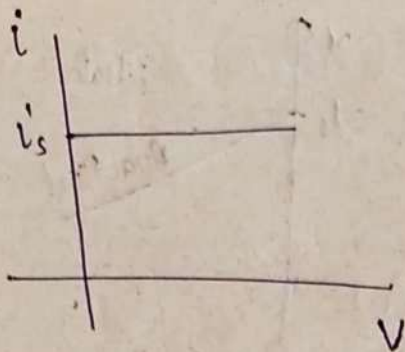

$$i = i_s$$

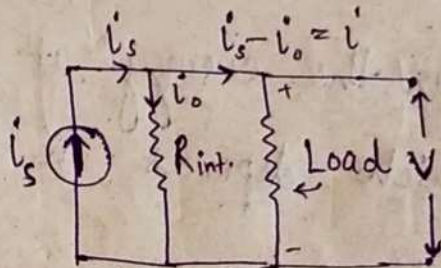



$$i = i_s - i_o$$

$$i = i_s - \frac{V}{R_{int}}$$



Pen down



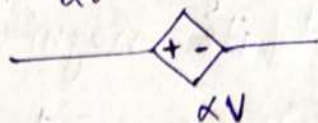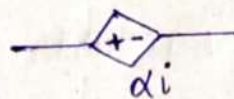
current controlled volt. src.  
voltage " " "




current " " "  
voltage " " "

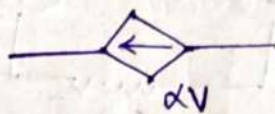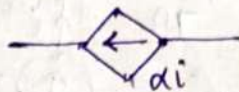


Note:

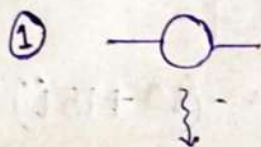

independent

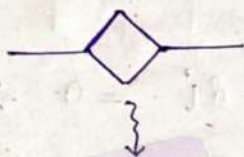

dependent

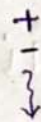


voltage

current

②  $\alpha \rightarrow$  constant and the current or voltage involved in deciding voltage / current source is given in problem.

③ Irrespective of voltage source, current remains same for one closed path.


ex:

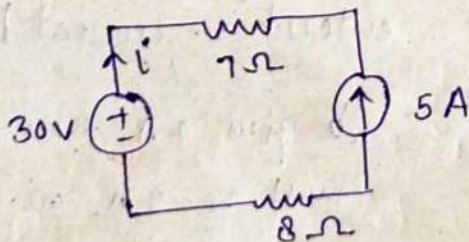

$$i = -5A$$
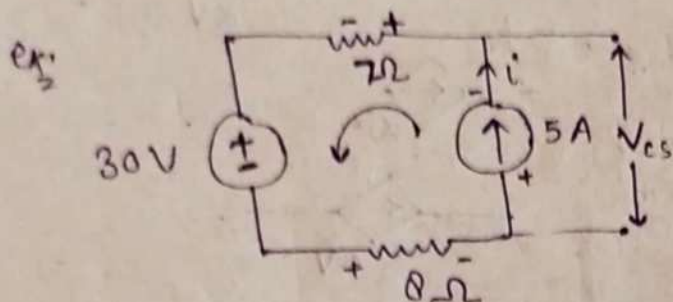
# If no current source is present in series with ideal indep. current source then current can't change in the circuit.

- ④ voltage across current source is never zero, and its magnitude is decided by external elements.



say  $V_{cs}$  is voltage across current source.


using KVL  $\rightarrow$

$$-V_{cs} - 7i - 30 - 8i = 0 \rightarrow V_{cs} = -(30 + 15i)$$


- ⑤ For // comb<sup>n</sup> of voltage sources, they must be same in order to obey KVL.

- ⑥ For series combination of current sources, they should be in same direc<sup>n</sup> to obey KCL.

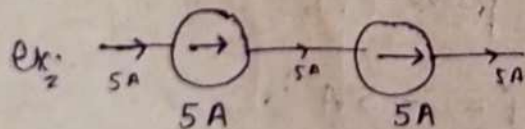If different magnitudes then, minimum will effectively flow.



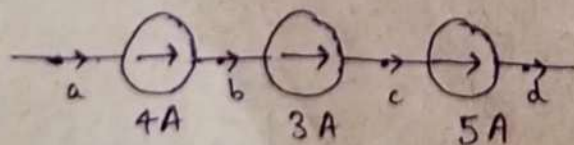KCL obeyed, current entered = current left



a gives 4A then c must be 4A acc. to KCL but 3A src. can't give 4A.

$$\therefore c = 3A$$

Now, 3A enters so at d we should get 3A (For KCL) & yes it can be possible becoz



5A src. can give 3A easily.  
now, at 'a' 3A enters so, 'b' must be 3A.  
which is again possible.

$\therefore$  overall current in the circuit = 3A

⑦ voltage src. in series and current srcs in parallel can be present without any restriction;

\* KCL and KVL  $\rightarrow$  within any loop,  $\sum (\text{voltage rise}) = \sum (\text{voltage drop})$   
or  $\sum (P.D \text{ across each component}) = 0$   
 $\sum (\text{All the currents at the junction}) = 0$   
Based on law of energy conservation  
using this  $\rightarrow$  consider incoming currents  $\ominus$  and outgoing currents  $\oplus$ .


or  $\sum (\text{incoming currents}) = \sum (\text{outgoing currents})$   
Based on law of conservation of charges.  
using this  $\rightarrow$  use as it is, as currents are given.



## • circuit v/s Network



Always  
closed path

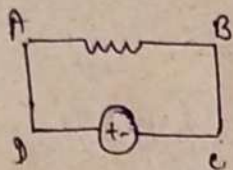

ABCD → circuit

ABEFA → circuit

BCDEB → "


ABCDEF → "

CMNDC → Network

ABCMNDEFA → "



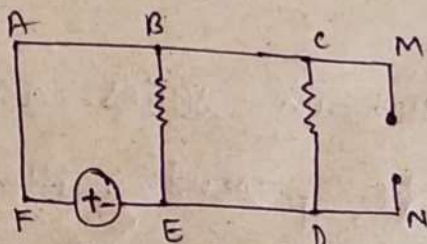May be closed or open or  
combination of both




Note: Every circuit is  
also a Network.

## • Node v/s Junction → a point where minimum 3 branches meet.



A point where minimum 2 branches meet.

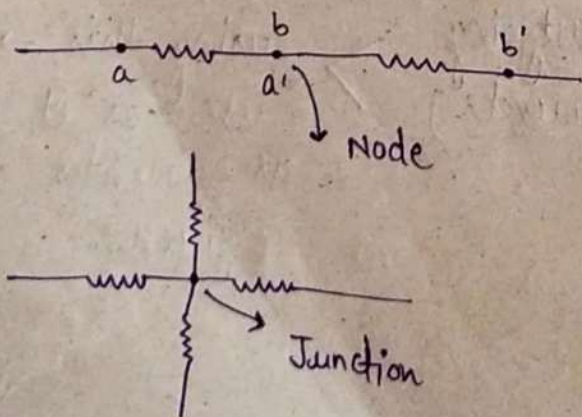


a, a', b, b' are the  
ends of a component.  
These are called as terminals



- Loop v/s Mesh  $\rightarrow$  The simplest loop which can't be further reduced.

$\downarrow$   
any closed path in which current can flow

ex:

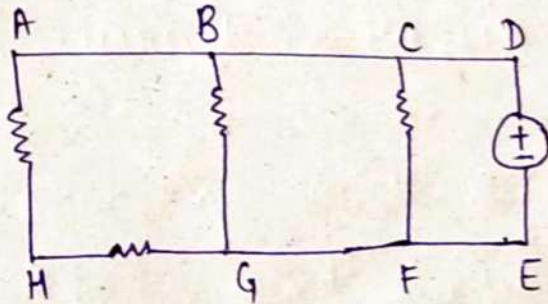

ABGHA, BCFGB, CDEFC  $\rightarrow$  Meshes

ABCFGHA, BCFGHB, ABCDEFGHA  $\rightarrow$  loops

Pen down


Q:


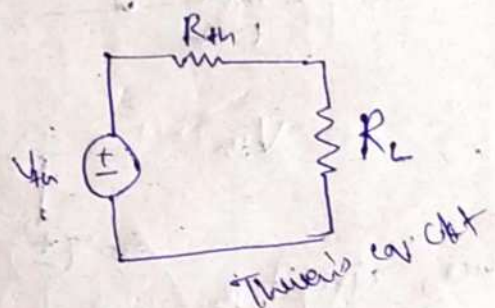
# Thevenin's Theorem :



↳ a linear bidirectional 2 terminal network can be replaced by an eq. network consisting of  $V_{th}$  connected in series with  $R_{th}$ .

- depend src  $\rightarrow$  as it is
- $V_{th} \rightarrow$  open circuit at  $R_L$  and find  $V_{th}$ .
- $R_{th} \rightarrow$  independ. src. are replaced by their int. resistances. and open circuit at  $R_L$ .



\* When independent src. are present  $\rightarrow$  attach a 1V indep. src in place of ~~load~~  $\rightarrow$  draw current 'i' from it then  $R_{th} = \frac{1}{i}$  (calculate i using any method)

Q. 2 for  $V_{th}$ ,

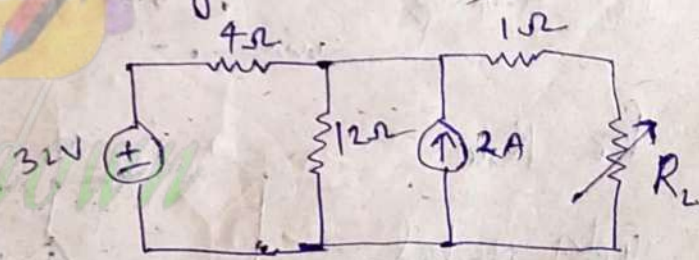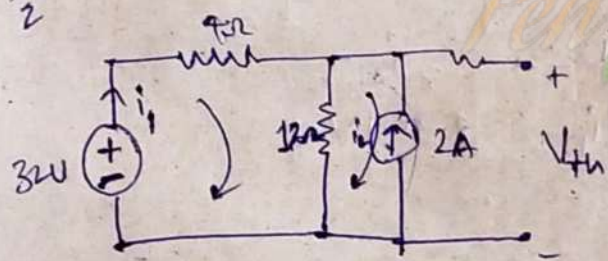

$$i_2 = -2A \quad \text{--- (2)}$$

$$32 - 4i_1 - 12(i_1 - i_2) = 0$$


$$32 - 16i_1 + 12i_2 = 0$$

$$0 - 4i_1 + 3i_2 = 0 \quad \text{--- (1)}$$


$$\therefore 0 - 4i_1 - 6 = 0 \Rightarrow i_1 = 0.5A$$

$$\therefore V_{th} = V_{12\Omega} = 12(i_1 - i_2) = 12 \times 2.5 = 30V$$

For  $R_{th}$  ?

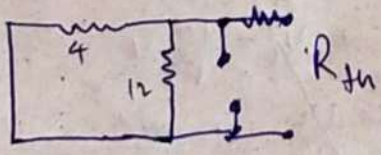

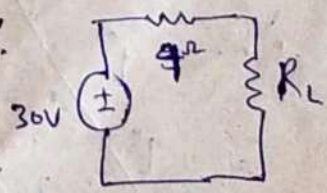
$$R_{th} = 4 + \frac{12 \times 12}{12 + 12} = 10\Omega$$



Thevenin's eq. ckt




Q. \*\*\*

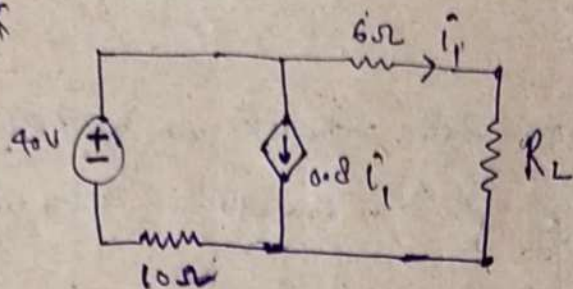


$V_{th}, R_{th}?$

for  $V_{th}$

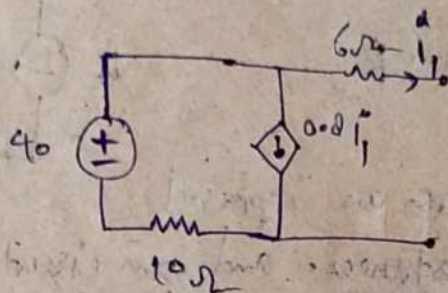


Since, circuit is open so  $i_1 = 0$

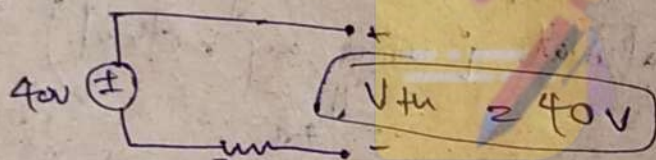$\therefore$  current through dep. src.  $= 0$



for  $R_{th}$

apply nodal analysis.

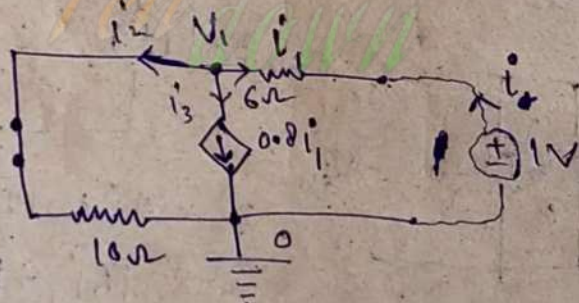

$$i_1 + i_2 + i_3 = 0 \Rightarrow \frac{(V_1 - 1)}{6} + \frac{V_1 - 0}{10} + 0.8i_1 = 0$$

~~$V_1 = 1$~~

$$\frac{V_1 - 1}{3} + \frac{V_1}{10} = 0$$

$$i = -i_1 =$$

$$i_2 = \frac{1}{26} A$$

$$R_{th} = 26 \Omega$$

$$10V_1 - 10 + 3V_1 = 0$$

$$13V_1 = 10 \Rightarrow V_1 = \frac{10}{13} V$$

$$\frac{1 - V_1}{6} = \frac{1 - \frac{10}{13}}{6} = \frac{3}{13 \times 6}$$




$$\frac{V_1}{10} + 1.8 i_1 = 0$$

$$\frac{V_1}{10} + \frac{1.8}{10} \times \frac{(V_1 - 1)}{6} = 0 \Rightarrow 4V_1 = 3 \Rightarrow V_1 = \frac{3}{4} \text{ V}$$

$$\therefore i_1 = \frac{\frac{3}{4} - 1}{6} = -\frac{1}{24} \text{ A}$$


$$I = -i_1 = \frac{1}{24} \text{ A}$$

$$\therefore R_{th} = 24 \Omega$$

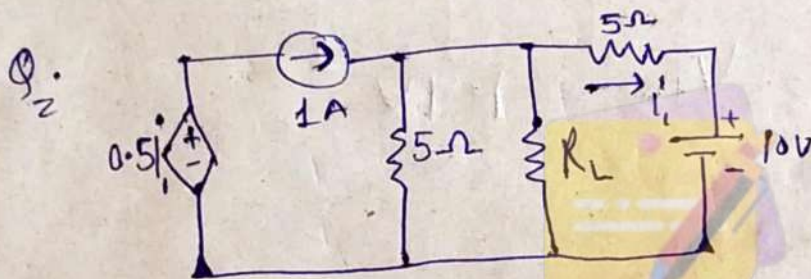

Find  $V_{th}$  &  $R_{th}$

For  $V_{th}$

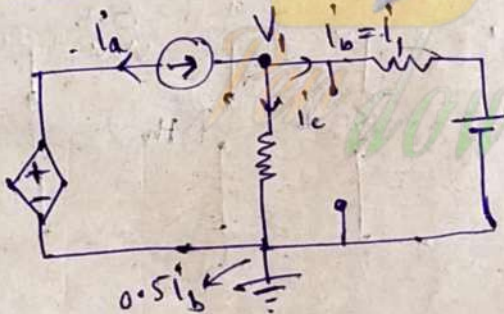

KCL at node ①

$$i_a + i_b + i_c = 0$$

$$-1 + \frac{V_1 - 10}{5} + \frac{V_1}{5} = 0$$

$$V_1 = 7.5 \text{ V}$$

$$\therefore V_{th} = \frac{1.5 \times 3}{2 \times 5} = 1.8 \text{ V}$$

$$\therefore V_{th} = 1.8 \text{ V}$$

$$-1 + \frac{(V_1 - 10)}{5} + \frac{V_1 - 0.5 i_b}{5} = 0$$

$$= i_b + \frac{V_1 - \frac{i_b}{2}}{5} = 1 \Rightarrow \frac{2V_1 - i_b}{10} + i_b = 1$$

$$2V_1 + 9i_b = 10 \Rightarrow 2V_1 + 9 \times \frac{(V_1 - 10)}{5} = 10$$

$$10V_1 + 9V_1 - 90 = 50$$

$$19V_1 = 140 \Rightarrow V_1 = \frac{140}{19} \text{ V}$$

$$\therefore V_{th} = 5 \times i_c = 5 \times \frac{15}{19} = \frac{75}{19} \text{ V}$$





from Q.

$$V_1 = V_{th} = \underline{7.4V}$$

for  $R_{th}$  ?

clearly  $R_{th} = \underline{\underline{\frac{5\Omega}{2}}}$

$$R_{th} = 2.5\Omega$$

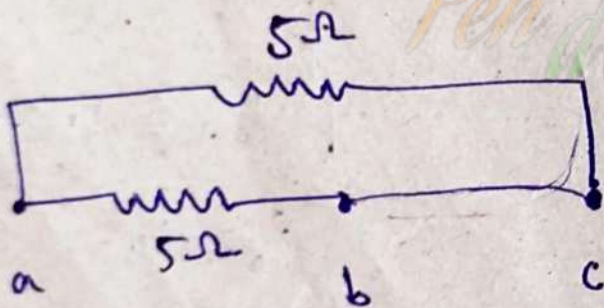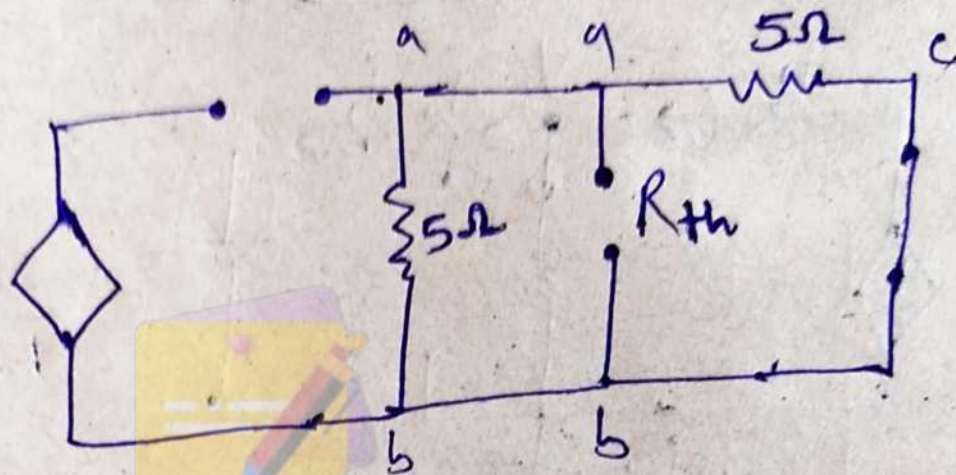




Norton's theorem : { same as Thevenin only diff. in  $I_N$  &  $V_{th}$  }

a linear & bidirectional 2 terminal network can be replaced by an equivalent circuit consisting of a current source  $I_N$  in parallel with a resistor  $R_N$ .


•  $R_N \rightarrow$  same as  $R_{th}$

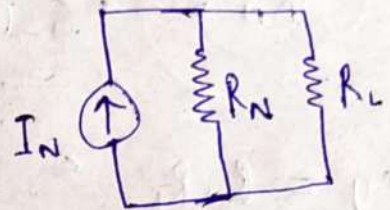•  $I_N \rightarrow$  short circuit load branch  
Solve for currents.  $I_N =$  current in load branch



as  $R_N = R_{th}$  ,  $I_N = \frac{V_{th}}{R_{th}}$  or  $R_{th} = R_N = \frac{V_{th}}{I_N}$

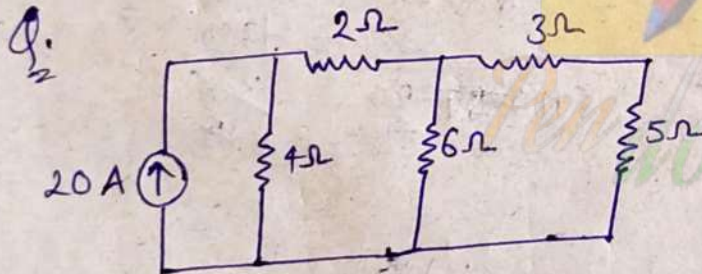{ this is source transformation technique }



Find current throy 5Ω  
using Norton's thero



→ so, let  $R_L = 5\Omega$

using current div. rule,

$i_2 = 10A = i_1$


$i_3 = \frac{10 \times 8}{8+3} = \frac{20}{3} \Rightarrow 6.67A$

$i_3 = I_N = 6.67A$

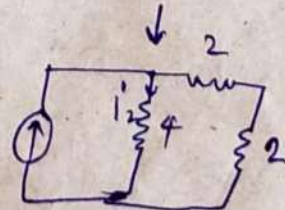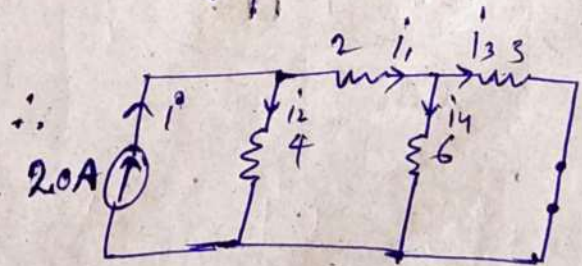



for Norton's resistance i.e.  $R_N$ .

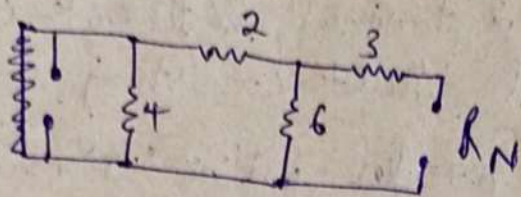

$$R_N = 6 \Omega$$

$$R_1 = 6 \Omega$$



$$R_{eq} = \frac{R_N R_L}{R_N + R_L}$$

$$= \frac{6 \times 5}{11} = \frac{30}{11} \Omega$$


No need =

$$\therefore I_{Load} = \frac{R_N \times I_N}{R_N + R_L} = \frac{6 \times 20}{11 + 5} = \frac{120}{16} = \frac{15}{2} A$$

$$I_{5\Omega} = \frac{40}{19} A$$



Note: Sawice transformation technique:

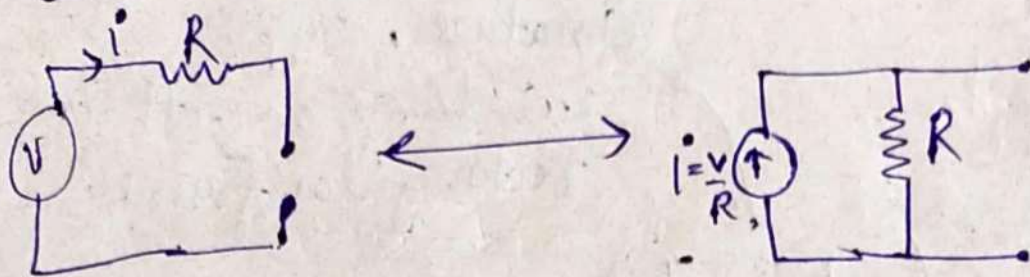



### Maximum Power Theorem

Maximum power from a network is delivered from a network ~~when~~ then resistance of load must be equal to the thevenin's resistance of network.

$$R_L = R_{th}$$



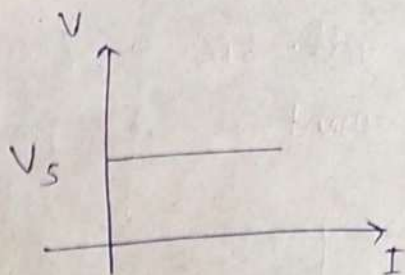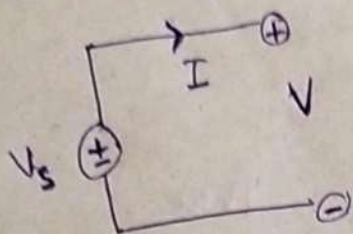
ideal volt. source  $\rightarrow R_{int} = 0$



delivers energy  
at specific constant voltage  
which doesn't depend on  
current I produced from  $V_s$ .

Practical volt. source


$R_{int} = \text{finite} = r$

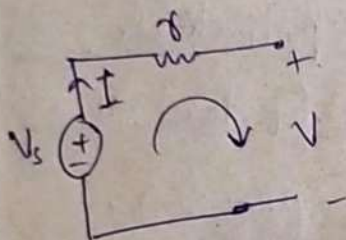


$$\sum \Delta V = 0$$

$$V_s - IR + V = 0$$

$$V = -IR + V_s$$


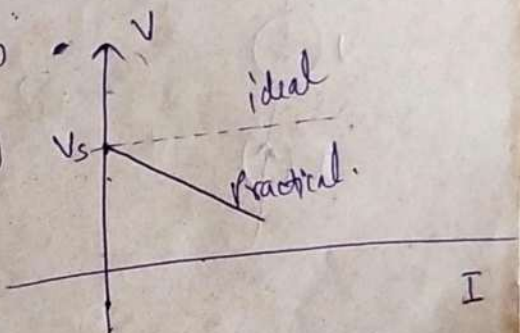


ideal & practical current source

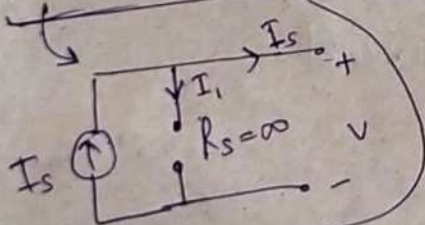


$$I = I_s$$

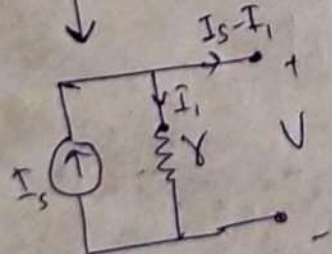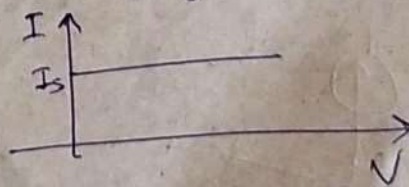delivers energy at a specific  
current indep. of. volt. across source



$$KVL =$$



$$I = I_s - \frac{V}{R_s}$$

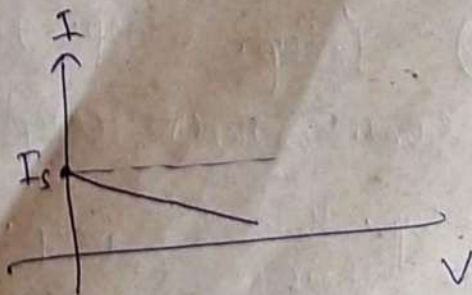




\* volt. src  $\rightarrow$  series  $\rightarrow$  add kr sakte hain.

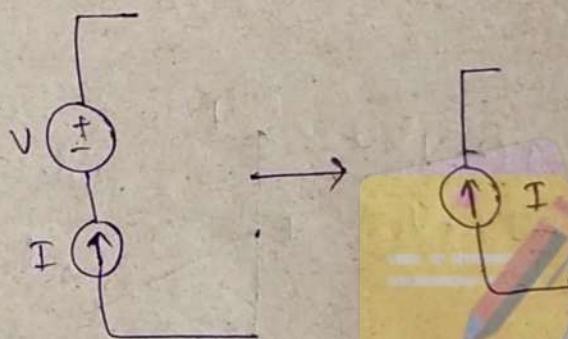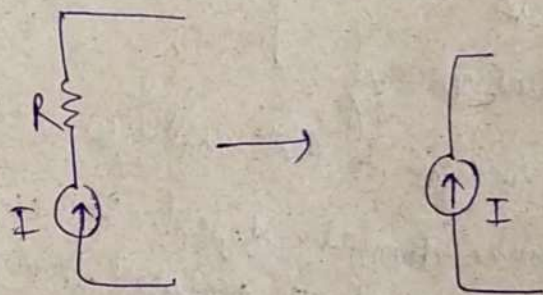\* current  $\rightarrow$  parallel  $\rightarrow$  \_\_\_\_\_



These conversions are only applicable for load side parameters.

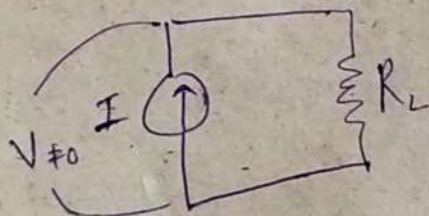① current src. doesn't have zero voltage across its terminals while providing fixed current.



② indep. & dep. sources are handled in same manner, except:

- ① Sup. then
- ② Thevenin's
- ③ Norton

indep.  $\rightarrow$  Replace by  $R_{int}$  } ideally, for  
 dep.  $\checkmark$  (no change) }  $V, R_{in} \neq 0$   
 $1, R_{in} \rightarrow \infty$



KCL

entering = +ve  
outgoing = -ve

then

$$\sum I = 0$$

KVL

$\ominus \rightarrow \oplus$   
low to high


(Rise)

$\oplus \rightarrow \ominus$

(drop.)

$$\sum \Delta V = 0$$

Q. \*\*\*

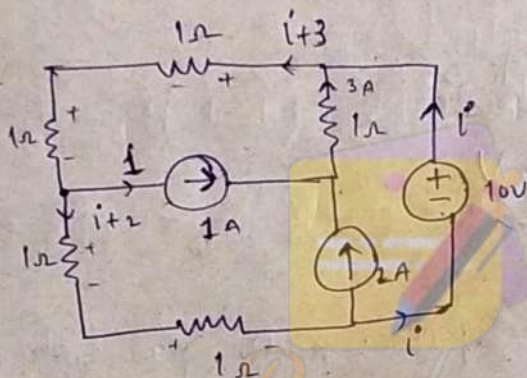

to avoid dealing with current sources, because we don't know volt. across them, we choose outer loop. & apply KVL  $\rightarrow$   
 $\sum \Delta V = 0$


$$+10 - (i+3) - (i+3) - (i+2) - (i+2) = 0$$

$$10 - 2[i+3] - 2[i+2] = 0$$

$$10 - 2(2i+5) = 0 \Rightarrow i = 0 \text{ A}$$



Q<sub>2</sub>

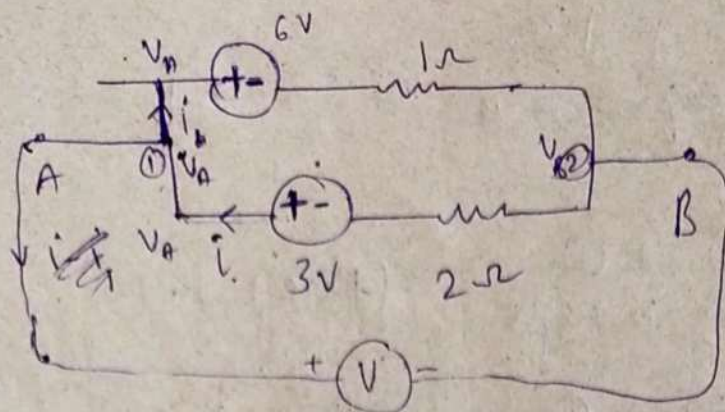



$V_{AB} = ?$

$$3 - 2i - V = 0$$

$$-6 - i_1 - 2i + 3 = 0$$

$$(6 + i_1) = V$$

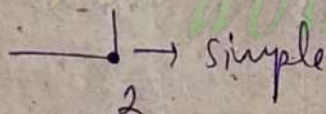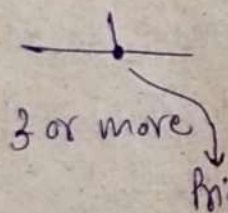\* current div. keval princ. node par hota hai.



in above circuit ①, ② are simple nodes

$$\cancel{3V = 0}$$

$$-6 - i - 2i + 3 = 0$$

$$-3 = 3i \Rightarrow i = 1A$$

Now

$$V_A - 6 - i = V_B$$

$$\{ V_A - V_B = 6 + i \Rightarrow 6 + 1 = 5V \}$$

open path me potential drop kabhi zero nahi hoga  
 $\therefore A \rightarrow B$  mey drop hote hue eqn ye banegi



# mesh analysis :


→ not applicable in non planar networks.

→ No. of eqn. to solve a network

$$C = M = b - (n - 1)$$

no. of eqn.      no. of meshes      no. of nodes      no. of branches

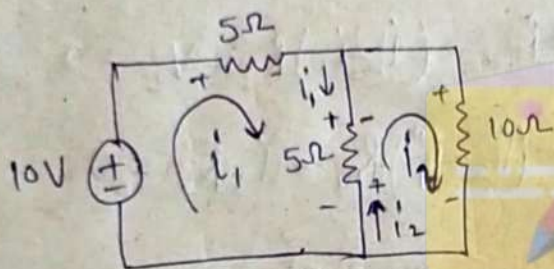→ take direction always clockwise for simplicity.



**for common branch \*\***

jis mesh ka analysis kar rache ho, usi ke current ko greater mano. aur uski direction ke according eqn likho.

Mesh ①:

$$10 - 5i_1 - 5(i_1 - i_2) = 0$$

$$10 - 5i_1 - 5i_1 + 5i_2 = 0 \Rightarrow 10 + 5i_2 - 10i_1 = 0 \quad \text{①}$$

mesh ②:

$$-5(i_2 - i_1) - 10i_2 = 0 \Rightarrow -5i_2 + 5i_1 - 10i_2 = 0$$

$$5i_1 = 15i_2 \quad \text{②}$$


$$i_1 = 3i_2$$

using ① & ② →

$$10 + 5i_2 - 10(3i_2) = 0 \Rightarrow i_2 = \frac{10}{25} \Rightarrow 0.4 A$$

$$i_1 = 1.2 A$$



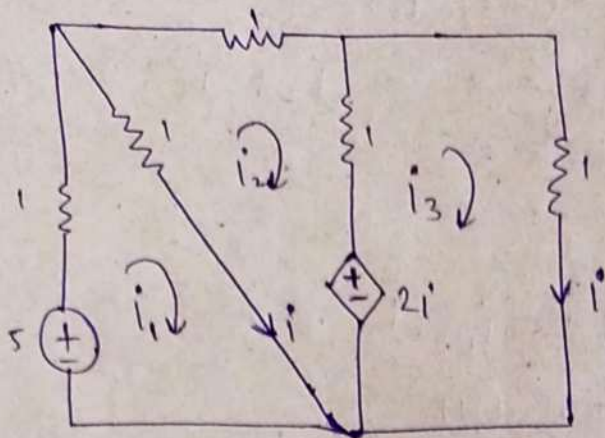

mesh ①:

$$5 - i_1 - (i_1 - i_2) = 0$$

mesh ②:

$$5 - 2i_1 + i_2 = 0 \quad \text{--- ①}$$

$$\left. \begin{array}{l} i = i_1 - i_2 \\ \text{or} \\ i_2 - i_1 = -i \end{array} \right\}$$

$$-(i_2 - i_1) - i_2 - (i_2 - i_3) - 2i = 0$$

$$-i_2 + i_1 - i_2 - i_2 + i_3 - 2(i_1 - i_2) = 0$$

$$-3i_2 + i_1 + i_3 - 2i_1 + 2i_2 = 0 \Rightarrow i_3 - i_1 - i_2 = 0 \quad \text{--- ②}$$

mesh ③:

$$-i_3 + 2i - (i_3 - i_2) = 0$$

$$-i_3 + 2i_3 - i_3 + i_2 = 0$$

$$\left. \begin{array}{l} \text{Hence} \\ i_3 = i \end{array} \right\}$$

$$i_2 = 0$$

$$i_3 = i_1$$

$$i_1 = \frac{5}{2} \Rightarrow 2.5 \text{ A}$$

$$\therefore i = 2.5 \text{ A}$$

This mesh ko  
solve kar rahe ho  
uske according dekho  
dependent parameters.  
ka relation with  
variables.



when current src. is present in mesh.


case ①: shared by other meshes in circuit.

case ②: not super mesh analysis \*

$i_1 = 2A$  directly

Q. 2

Find  $i_3 = ?$

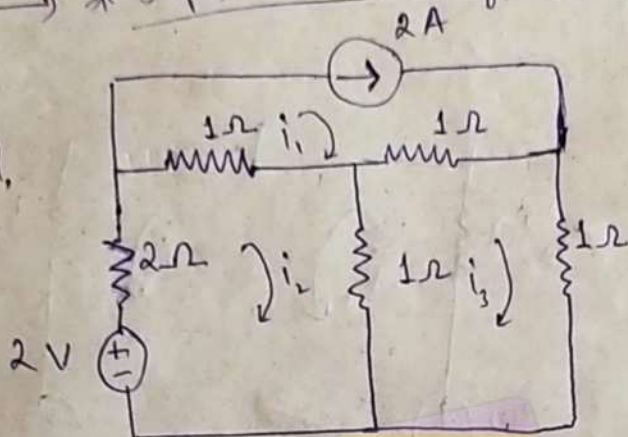

now,  $2 - 2i_2 - (i_2 - 2) - (i_2 - i_3) = 0$

$$i_3 + 2 - 4i_2 + 2 = 0$$

$$i_3 - 4i_2 = -4 \quad \text{--- (1)}$$

$$-(i_3 - i_2) - (i_3 - 2) - i_3 = 0$$

$$-3i_3 + i_2 + 2 = 0 \quad \text{--- (2)}$$

$$2 \times (1) + (2)$$

$$-11i_3 = -12 \Rightarrow i_3 = \frac{12}{11} A$$

mesh ①:

~~$-(i_1 - i_2) - (i_1 - i_3) = 0$~~

but  $i_1 = 2A$  directly

~~$-2 + i_2 - 2 + i_3 = 0 \Rightarrow i_2 + i_3 = 4$~~  (1)

mesh ②:

$$-(i_2 - i_1) - (i_2 - i_3) + 2 - 2i_2 = 0$$

$$-4i_2 + 4 + i_3 = 0 \Rightarrow i_3 - 4i_2 = -4 \quad \text{--- (1)}$$

$4 \times (1) + (2)$

~~$i_3 = 12/11$~~   $5i_3 = 12 \Rightarrow i_3 = 2.4 A$

~~$i_2 = 1.6 A$~~

mesh ②:


$$2 - 2i_2 - (i_2 - 2) - (i_2 - 2) = 0$$

$$2 - 4i_2 = -4 \Rightarrow i_2 = \frac{6}{4} = 1.5 A$$

$$\therefore i_3 = -4 + 4 \times 1.5 = 2 A.$$



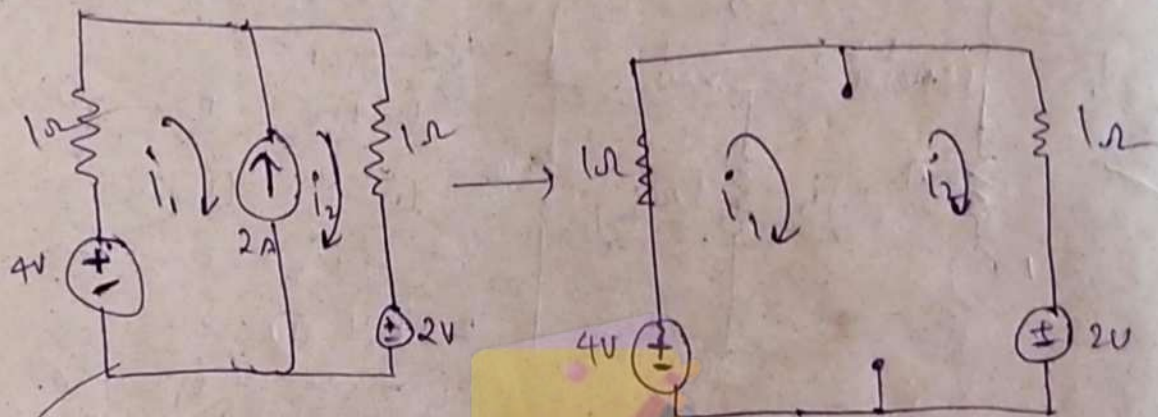
Super mesh: when a current src is present in b/w 2 meshes, we remove the branch having current src. and then solving. loop is known as ~~br~~ supermesh.



Now apply KVL →

$$4 - i_1 - i_2 - 2 = 0 \Rightarrow i_1 + i_2 = 2 \quad \text{--- (1)}$$

now

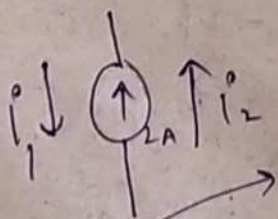

$$i_2 - i_1 = 2 \quad \text{--- (2)}$$


$$+ \quad i_2 = 2 \text{ A}$$

$$\therefore i_1 = 1 \text{ A}$$

$i_2$  ki direction me 2A hai so




Q. 2

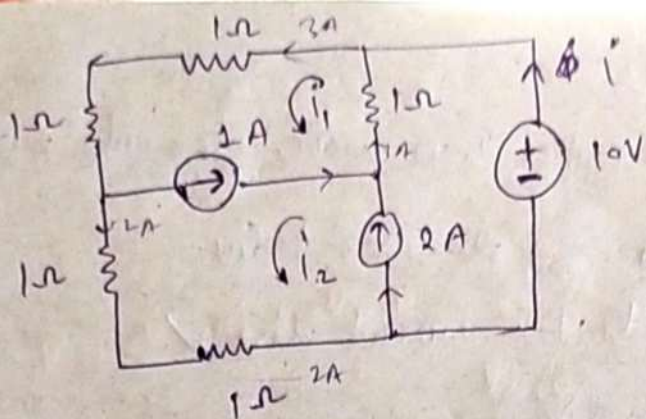

Solve using  
supermesh analysis

Find  $i'$ ?

→

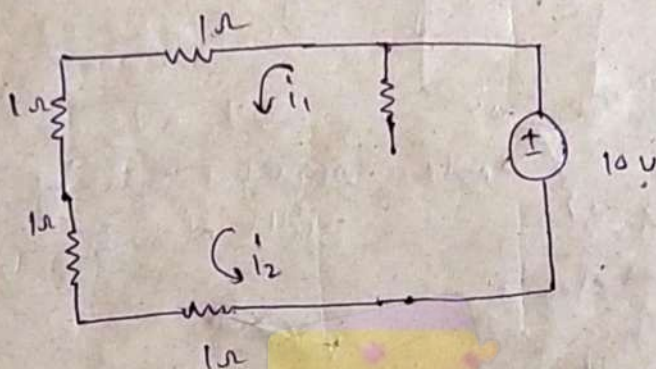

$$-i_1 - i_1 - i_2 - i_2 + 10 = 0$$

$$i_1 + i_2 = 5 \quad \text{--- (1)}$$

Now,

$$i_1 - i_2 = 1 \quad \text{--- (2)}$$

$$\therefore i_2 = 2A$$

$$\underline{i_1 = 3A}$$


$$\text{Implies } i' = 0A$$



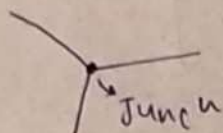
# Nodal analysis:

Node  $\rightarrow$  common point where 2 or more elements meet.

- Simple  $\rightarrow$  2 elements  $\rightarrow$  no current div.
- Principle  $\rightarrow$   $> 2$  elements  $\rightarrow$  current div ✓
- $\hookrightarrow$  considered in analysis.



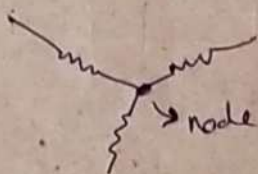simple branches  
may or may not have elements.




branches must be with elements

- identify total nodes
- assign voltage to each node, one node is taken as ref. node (datum). Take  $V_{\text{ref. node}} = 0$ 
  - Bottom node is often taken as ref.
- develop KCL eqn for each non-ref. node
- Solve KCL eqns to get  $V_{\text{node}}$ .

Note: ① for both planar & non-planar networks.

② No. of eqns  $e = N - 1$

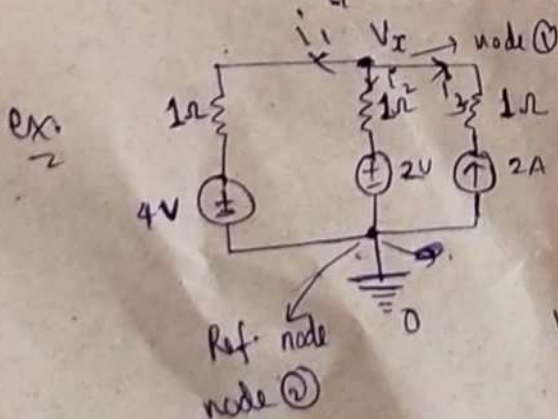

no. of nodes (Princ. Nodes)

KCL of non-ref node ①

$$\frac{V_x - 4}{1} + \frac{V_x - 2}{1} + (-2) = 0$$

entering (sum of leaving current = sum of entering current)

$$V_x = \frac{0}{2} = 4V.$$




When voltage src. is present:

case ①: voltage src connected b/w the ref. node & non-ref. node.

case ②: volt. \_\_\_\_\_ 2 non-ref. nodes.

→ Super node analysis.

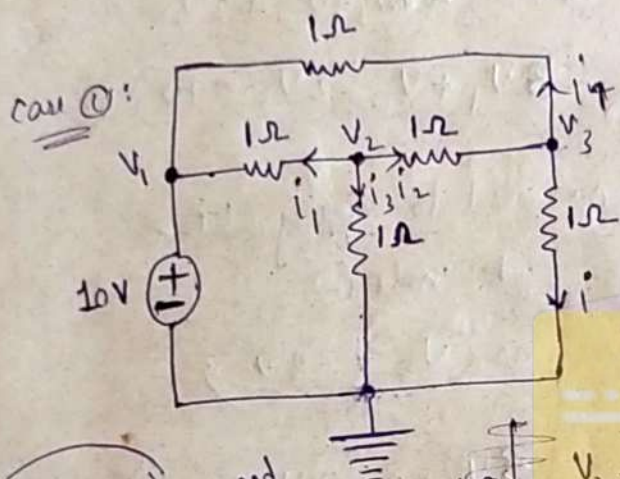

Find  $i$  using nodal analysis.

KCL at node ②:

$$i_1 + i_2 + i_3 = 0$$

outgoing      incoming

$V_1 = 10V$  no need to write KCL for node ①

KCL at node node ③

$$\frac{V_2 - V_1}{1} + \frac{V_2 - 0}{1} + \frac{V_2 - V_3}{1} = 0$$

$$V_2 - 10 + V_2 + V_2 - V_3 = 0$$

$$3V_2 - V_3 = 10 \quad \text{--- (1)}$$

$$i_2 = i_1 + i$$

$$\frac{V_2 - V_3}{1} = \frac{V_3 - 10}{1} + \frac{V_3 - 0}{1}$$

$$V_2 - V_3 = 2V_3 - 10 \Rightarrow 3V_3 - V_2 = 10 \quad \text{--- (2)}$$

$$\textcircled{1} \times 3 + \textcircled{2} : 8V_2 = 40 \Rightarrow V_2 = 5V$$

$$\therefore V_3 = 5V$$

$$\therefore i = 5A$$




$$\frac{12+2}{2} + \frac{26+2}{1} = i_x$$

$$i_x = 20 + 7 \Rightarrow 85 \text{ A}$$

$$\therefore P_{2V \text{ source}} = 2 \times i_x = \underline{\underline{70 \text{ W}}}$$


Q. (cont): super node analysis;

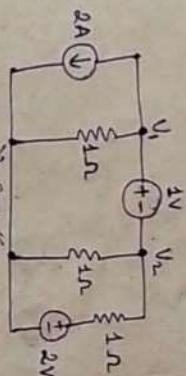

non-self. principal nodes so (1V) b/w them makes it a problem of super node analysis.


we have 3 nodes

node ① & ② are

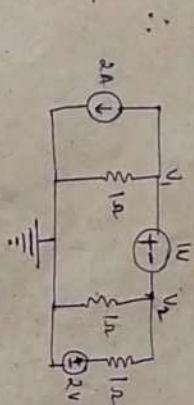

Here we need to apply KCL separately at node ①, ②.

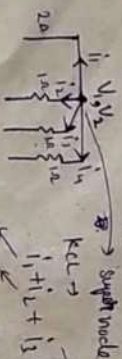but neglect the (1V) src. and make a common node known as super node and apply KCL at this node.



Consider  $V_1$   $2 + \frac{V_1 - 0}{1} + \frac{V_2 - 0}{1} + \frac{V_2 - 2}{1} = 0$

Consider  $V_2$   $i_1 + i_2 + i_3 + i_4 = 0$

Consider  $V_3$   $2 + \frac{V_1 - 0}{1} + \frac{V_2 - 0}{1} + \frac{V_2 - 2}{1} = 0$

So  $V_1 + 2V_2 = 0$  — (1)


node, by KVL in  $V_1 \xrightarrow{+} V_2$

$$V_1 - 1 = V_2 \Rightarrow V_1 - V_2 = 1 \quad \text{--- (2)}$$

$$\text{①} - \text{②} \quad 3V_1 = -1 \Rightarrow V_1 = -\frac{1}{3} \text{ V}$$

$$\therefore V_1 = -\frac{1}{3} \text{ V}$$

Q. 2

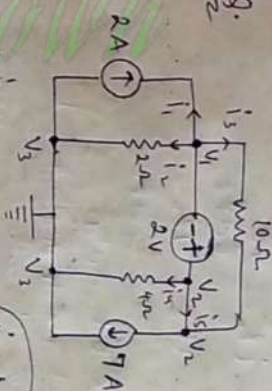

Find  $V_1, V_2$ ?

clearly we have only 3 nodes.

$$i_3 + i_5 = 7 \text{ nodes.}$$



$$i_1 + i_2 + i_3 + i_4 + i_5 = 0$$

$$-2 + \frac{V_1 - 0}{2} + \left( \frac{V_1 - V_2}{1} + \frac{V_2 - 0}{4} + \frac{V_2 - 2}{1} \right) + \frac{V_2 - 2}{1} = 0$$

$$-2 + \frac{V_1}{2} + \frac{V_1 - V_2}{1} + \frac{V_2 - 0}{4} + \frac{V_2 - 2}{1} = 0$$

$$2V_1 + V_2 = -20 \quad \text{--- (1)}$$

by KCL,  $V_1 + 2 = V_2 \Rightarrow V_2 - V_1 = 2 \quad \text{--- (2)}$

$$\text{①} - \text{②} \quad 3V_1 = -22 \Rightarrow V_1 = -\frac{22}{3} \text{ V}$$

$$V_2 = 2 - \frac{22}{3} = -\frac{16}{3} \text{ V}$$