

"Carey-Foster Bridge"

Objective :-

To determine the specific resistance of the material of a given unknown wire using 'Carey-Foster Bridge'.

Apparatus :- Carey-Foster bridge, power supply, resistance box, wire of unknown resistance, a thick copper strip, a plug key, two equal resistances, a galvanometer.

Theory :-

The specific resistance is defined as resistance of wire of unit length and unit cross-section area. Since, Resistance is proportional to the length and inversely proportional to the cross-section area, the specific resistance is defined as,

$$\rho = R(A) \text{ } \Omega\text{m} = R\left(\frac{\pi r^2}{l}\right) \Omega\text{m}$$

where l = length of given wire.

r = radius of cross section of given wire.

R = Resistance of given wire.

ρ = specific resistance.

Teacher's Signature: _____

The specific resistance (ρ) depends only on the material and is independent of shape of wire.

In order to determine specific resistance, we need to find resistance, length and radius of a given wire. The length and radius can be calculated using Vernier Caliper and screw-gauge. The measurement of resistance is carried out with this experiment.

Why Carey - Foster Bridge :-

An easier method to

determine resistance is as follow:

Attach a battery across the wire,

Note the voltage across the wire and current flowing through it.

Apply Ohm's law, $R = V/I$

you may have other simple techniques but

This method is not suitable for measuring low resistances because of the following reason:

Teacher's Signature: _____

When we join two conducting wires or two resistances by clamping or by twisting (and not by soldering), we actually bring two layers of molecules close to each other. The sheets of molecules have gap of few angstroms. The electrons in a conductor are assumed to move freely without losing any energy. When these electrons pass through the junction, they have to jump from one layer to other and they lose some energy in this process. The energy loss is equivalent to resistance, called 'Contact resistance'.

The value of contact resistance is small and can be safely neglected when we measure resistance of higher order. But for small resistance we can't neglect contact resistance.

So, we have to look for a method which eliminate or bypass the error in measurements due to contact resistance.

'Carey-Foster bridge' is one such device which is highly sensitive and can measure low resistance which avoid this error in measurements.

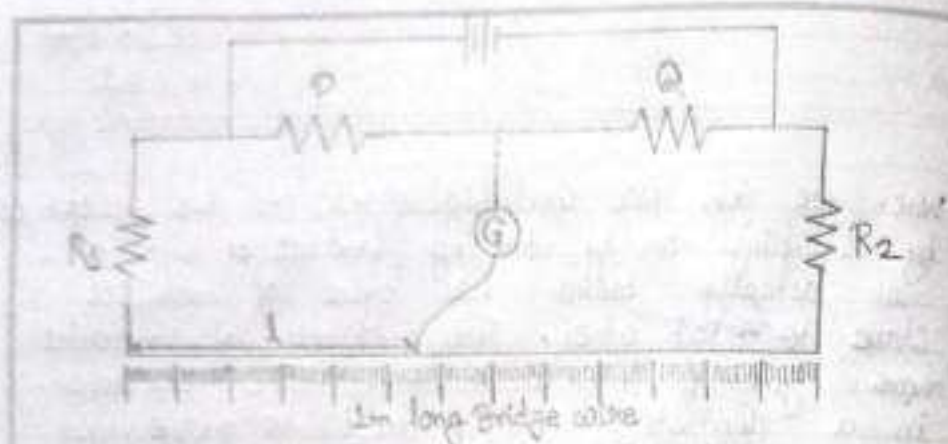


Figure 1: A schematic of Carey-Foster Bridge.

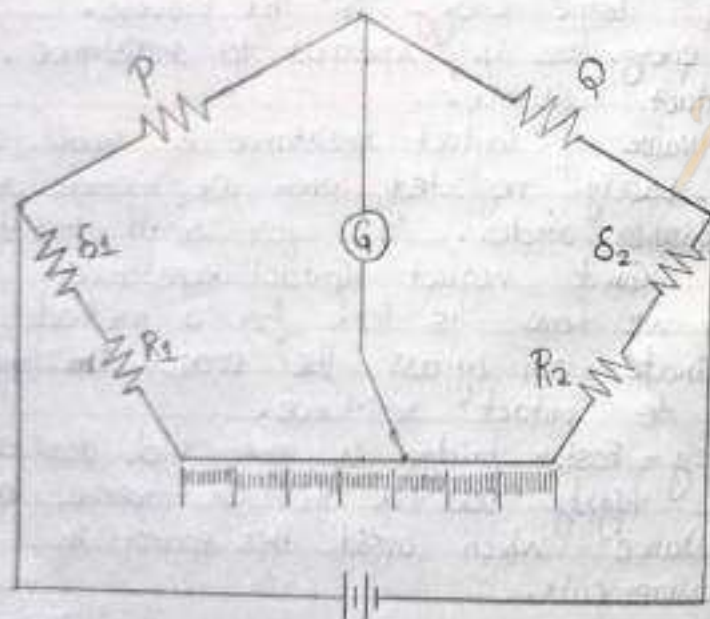


Figure 2: Another schematic of Carey-Foster Bridge. This figure shows the contact resistance through δ_1 and δ_2 .

Date 17-12-2021

Expt. No.

Page No. 94

Working Principle:-

The apparatus works on the principle of wheat-stone bridge.

Let's assume that the Contact resistance on the left and right hand side are equivalent to the resistance δ_1 and δ_2 respectively.

The Contact resistances δ_1 and δ_2 are unknown, small in value and there exist no way to measure them.

Our goal is to measure unknown resistance without evaluating δ_1 and δ_2 .

If we get null point, i.e. no current through galvanometer, at a distance l_1 from left, then we can write,

$$\frac{P}{Q} = \frac{R_1 + \delta_1 + R_w l_1}{R_2 + \delta_2 + R_w (1-l_1)} \quad \dots (1)$$

or

$$\frac{P}{Q} + 1 = \frac{R_1 + R_2 + \delta_1 + \delta_2 + R_w}{R_2 + \delta_2 + R_w (1-l_1)} \quad \dots (2)$$

Teacher's Signature: _____

where R_w is the resistance per unit length of bridge wire.

The bridge wire is 1m long.

If we interchange R_1 and R_2 , we get new position of null point at $l = l_2$, so we now have,

$$\frac{P}{Q} = \frac{R_2 + \delta_1 + R_w l_2}{R_1 + \delta_2 + R_w (1 - l_2)} \quad \text{--- (3)}$$

OR

$$\frac{P}{Q} + 1 = \frac{R_1 + R_2 + \delta_1 + \delta_2 + R_w}{R_1 + \delta_2 + R_w (1 - l_2)} \quad \text{--- (4)}$$

from equⁿ (2, 4) we get,

$$R_1 - R_2 = R_w (l_2 - l_1) \quad \text{--- (5)}$$

Thus we have a relation independent of δ_1 and δ_2 . we shall use this expression to determine unknown resistance.

Teacher's Signature: _____

Procedure :-

We have Eq. (5) two times to determine unknown resistance.

First we evaluate R_w . we set following values for different resistances.

$$P = 1\Omega$$

$$Q = 1\Omega$$

$$R_1 = \text{Resistance box}$$

$$R_2 = \text{Copper strip} = 0.02$$

we can find null point. Let's assume that null point is found at $l = l_1$.

Now we interchange R_1 and R_2 , let's assume that new position of null point is $l = l_2$. from eq. (5), we get,

$$R_1 - 0 = R_w (l_2 - l_1) \quad \text{--- (6)}$$

or

$$R_w = \frac{R_1}{(l_2 - l_1)} \text{ m/m} \quad \text{--- (7)}$$

Teacher's Signature: _____

Once R_w is evaluated, we use Eq. (5) again to determine unknown resistance.
Now we set following values for resistances:

$$P = 1 \Omega \text{ (same as before)}$$

$$Q = 1 \Omega \text{ (same as before)}$$

$$R_1 = \text{Resistance box (same as before)}$$

$$R_2 = \text{Unknown resistance} = R \Omega$$

we again find null point. Let's assume that null point is found at $l = l_1'$ after interchanging R_1 and R_2 , i.e.

$$R_1 = \text{Unknown resistance} = R$$

$$R_2 = \text{Resistance box}$$

if new position of null point is $l = l_2'$ then from eq. (5), we get,

$$R_1 - R = R_w (l_2' - l_1')$$

or

$$R = R_1 - R_w (l_2' - l_1')$$

The Unknown resistance can be calculated from above expression after substituting R_w from Eq. (7).

Teacher's Signature: _____

Observations :-

T-1 Determination of resistance per unit length of bridge wire, $R_w \Omega/\text{cm}$:

$P = 1\Omega$, $Q = 1\Omega$, $R_1 = \text{Resistance box}$, $R_2 = \text{Copper strip} = 0\Omega$

S.No.	$R_1 (\Omega)$	$l_1 (\text{cm})$	$l_2 (\text{cm})$	$(l_2 - l_1)$ (in cm)	$R_w = \frac{R_1}{(l_2 - l_1)}$ (Ω/cm)	Mean value of R_w
1	0.2	41.8	60.1	18.3	0.011	0.0164 Ω/cm
2	0.5	33.9	66.1	32.2	0.015	
3	1.0	20.5	77.9	57.4	0.017	
4	1.2	20.2	80.4	60.2	0.019	
5	1.5	15.0	85.6	70.6	0.021	

T-2 Determination of Unknown resistance, R :

$P = 1\Omega$, $Q = 1\Omega$, $R_1 = \text{Resistance box}$, $R_2 = \text{Unknown Resistance} = R\Omega$

S.No.	$R_1 (\Omega)$	$l_1' (\text{cm})$	$l_2' (\text{cm})$	$(l_2' - l_1')$ (cm)	$R = R_1 - R_w(l_2' - l_1')$ (Ω)	Mean value of R
1	0.5	53.0	58.5	5.5	0.410	0.618
2	0.7	47.3	52.4	5.1	0.618	

Teacher's Signature: _____

Date 17-12-2021

Expt. No.

Page No. 09

S.No	$R_1(\Omega)$	$l_1'(cm)$	$l_2'(cm)$	$(l_2' - l_1')$	$R = R_1 - R_w(l_2' - l_1')$	Mean value of R
3	1.0	35.7	61.8	26.1	0.572	0.642 Ω
4	1.2	35.0	64.3	29.3	0.720	
5	1.5	32.7	69.8	37.1	0.892	

T-3 Measurement of the radius of the cross-section of unknown resistance wire:

Zero error = -20

Least count of screw gauge = 0.001 cm

S.No	Measurement along any direction.			Measurement along perpendicular direction.			Diameter	Mean diameter	Mean radius
	MS (cm)	CS (cm)	Total a (cm)	MS (cm)	CS (cm)	Total b (cm)	$d = \frac{a+b}{2}$	(d) (in cm)	$(r = \frac{d}{2})$ (in cm)
1	0	34	0.054	0	29	0.049	0.0515	0.051	0.026 cm
2	0	32	0.052	0	30	0.050	0.051		
3	0	35	0.055	0	28	0.048	0.051		

Zero error correction = $20 \times 0.001 \text{ cm}$
 = 0.02 cm

Teacher's Signature: _____

Zero error correction = 0.02 cm
that is already applied in T-3.

T-4 Length of wire = 19.3 cm

Calculations:-

From observation, we have

Unknown resistance $R = 0.642 \Omega$

radius of the wire = 0.026 cm = $0.026 \times 10^{-2} \text{ m}$

length of the wire = 19.3 cm = $19.3 \times 10^{-2} \text{ m}$

$$\rho = R \left(\frac{A}{l} \right) = R \left(\frac{\pi r^2}{l} \right) = \frac{0.642 \times 3.14 \times (0.026 \times 10^{-2})^2}{19.3 \times 10^{-2}}$$

$$\rho = 6.86 \times 10^{-7} \Omega \text{ m}$$

Results:-

The specific Resistance of the material of given wire is $6.86 \times 10^{-7} \Omega \text{ m}$.

Precautions:-

- 1) All the connections are to be made tightly.
- 2) Allow the current to flow when the readings are to be taken.
- 3) Jockey should not be dragged on wire, it should be lifted and made in contact with the wire.

Teacher's Signature: _____