CT & PT

DET = Current Transformer (used to measure current)

DPT = Rotential Transformer (" high voltage)


3 CT & PT. is always used in AC

December statio in CT = 1000/5


BCT & PT asie installed in good in substation.

Cusount Fromformer - OIT is an instrument transformer used for measurement of high curo a string: 500/s, 500/s, 1000/s noots used or ct. (IN=IzN2)

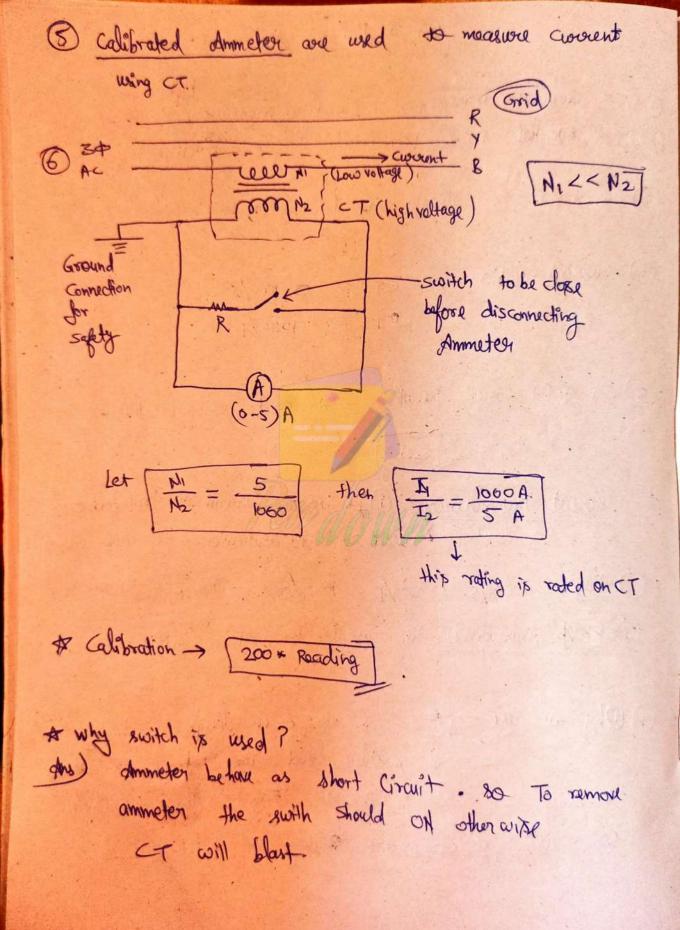
(4) the size at Cost of (A) will very large a expensive so use a cost of (A) will very large a expensive



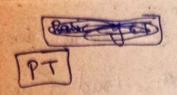(a) CT is designed who I shortest Load (mayor I bassed) as ct depend on Load (assuent varies per bad) CT will measure O if Load = 0 CT is sonia to load.



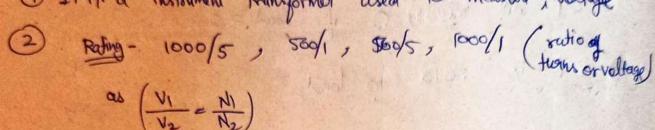1) It is a sustrament Transformer used to measure, voltage



3) step down Transformer ix used


4 Smecked in parallel to load

As the Patornal resistance of $V = \infty$ so terminal pot. Can be measured by proper calibration.

of shewo

* bot transformer terminals can be left open no havem (c & p)

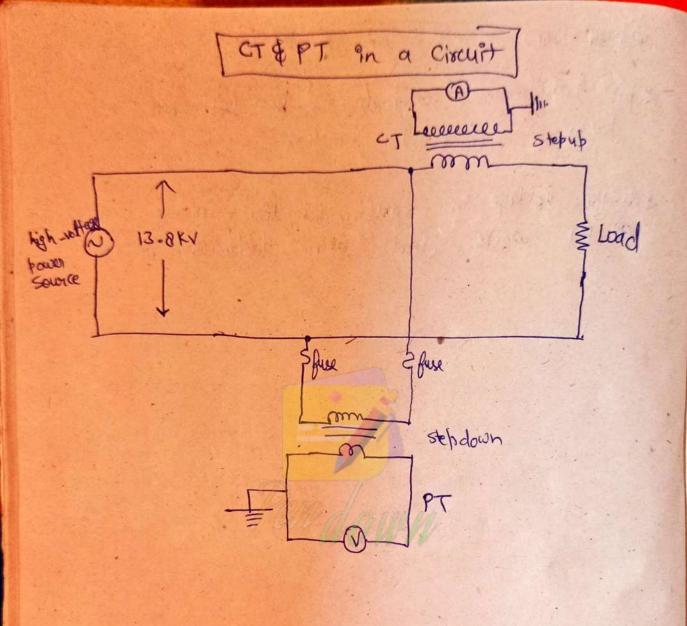
Ads the voltage in transformation line remains constant so PT works good even fluctuations in load



Phasor for CT

Let 4= + Nin wt
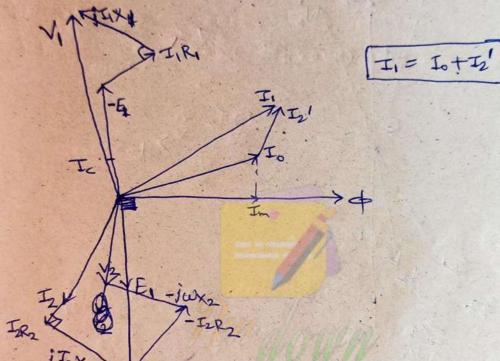
$$E_2 = -\frac{d\Phi}{dt} = -\Phi_0 \omega_{COS} \omega t = E_0 sin(\omega t - \pi/2)$$



Phapor for P V2'= emis Minox

ORatio escenor
ORatio everor
De Phase angle courses
T course T
1 Ratio - everon:
No The due to magnetizing & Gre loss
/ Ratio everon = Nominal natio - actual natio x100 actual natio
$\frac{h}{h} = \frac{h}{h} \times 100$
②Phase angle ouron - 芸 x100
Iz & It has phase shift of 180° but not actually
Sound due to magnetizing & . Gra loss & those angle is \$180°
phase angle escreen (0) = $\frac{180}{11}$ [$\frac{\pm m(oss)}{nIs}$]
0= Im(058 - Icsin 8 in sadiany indegree

% ratio evocor =
$$\frac{K_1 - R_1}{R_1} \times 100$$

$$= \frac{N_1}{N_2} - \frac{V_1}{V_2} \times 100$$

$$= \frac{V_1}{V_2} \times 100$$

they angle everon -. Vp & Vs, not has any phase alight but due to may & Gre toss loss comes as phase angle in PT

To (XPGSA - RpsinA) + Texp-Indip